
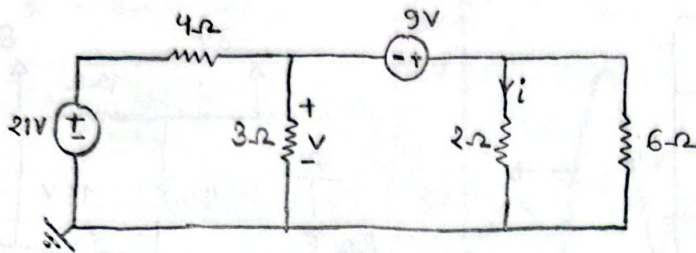


Answer to the Question No-1

(a)

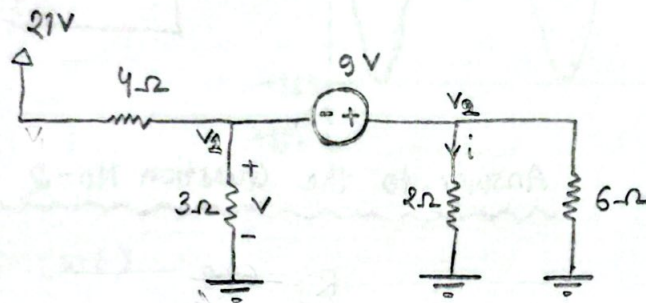

(b)

KCL on V_1 & V_2

$$\frac{V_1 - 21}{4} + \frac{V_1 - 0}{3} + \frac{V_2 - 0}{2} + \frac{V_2 - 0}{6} = 0$$

$$\Rightarrow 3V_1 - 63 + 4V_1 + 6V_2 + 2V_2 = 0$$

$$\Rightarrow 7V_1 + 8V_2 = 63 \quad \text{--- (1)}$$

Supernode relation,

$$-V_1 + V_2 = 9 \quad \text{--- (2)}$$

Solving (1) & (2)

$$V_1 = -0.6 \text{ V}$$

$$V_2 = 8.4 \text{ V}$$

Now,


$$V = V_1 - 0$$

$$= -0.6 - 0$$


$$\therefore V = -0.6 \text{ V}$$

$$i = \frac{V_2 - 0}{2} = \frac{8.4 - 0}{2}$$

$$\therefore i = 4.2 \text{ A}$$

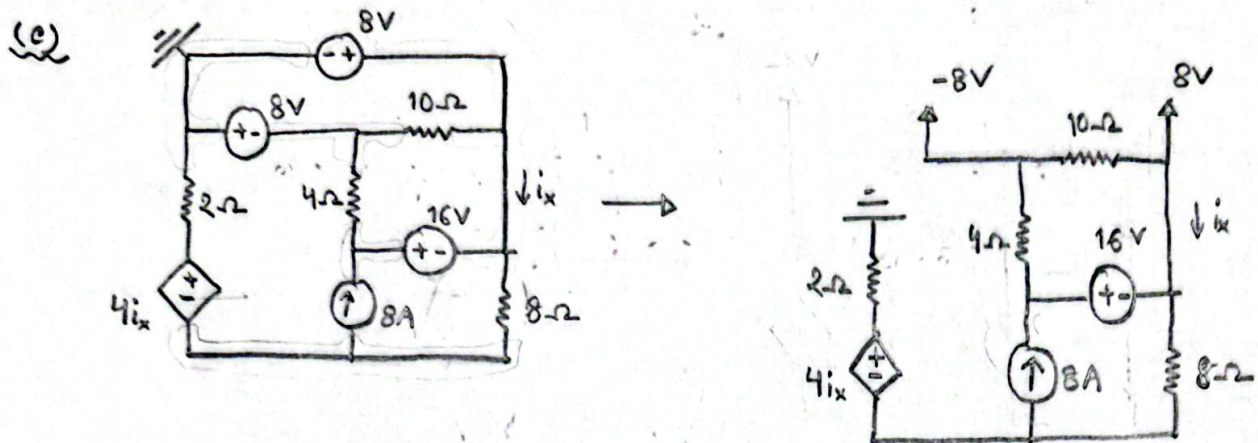

Answer to the Question No-2

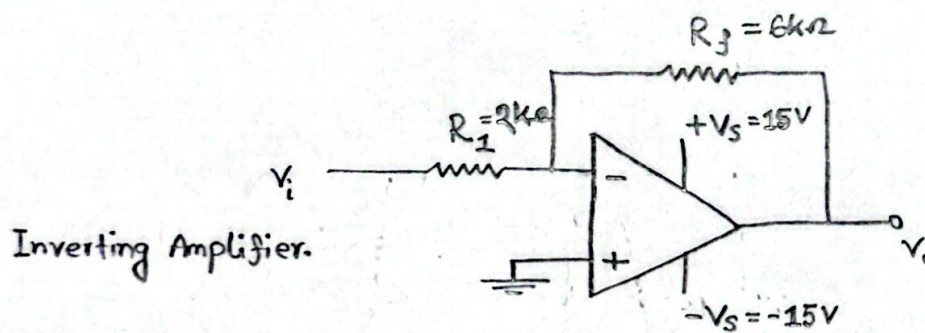

(a) $V_i = 4V$

We know, $V_o = -\frac{R_f}{R_1} V_i$

$$= -\frac{6}{2} \times 4$$


$$= -12V$$

(b) $V_i = 4 \sin(\omega t)$

$$V_o = -\frac{R_f}{R_i} V_i$$

$$= -\frac{6}{2} \times 4 \sin(\omega t)$$


$$= -12 \sin(\omega t)$$

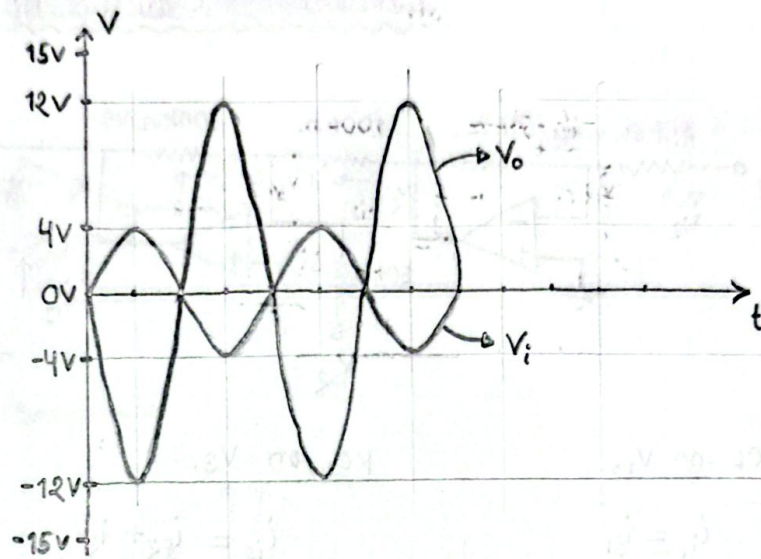


(c) $V_i = 6 \sin(\omega t)$

$$V_o = -\frac{6}{2} \times 6 \sin(\omega t)$$

$$= -18 \sin(\omega t)$$

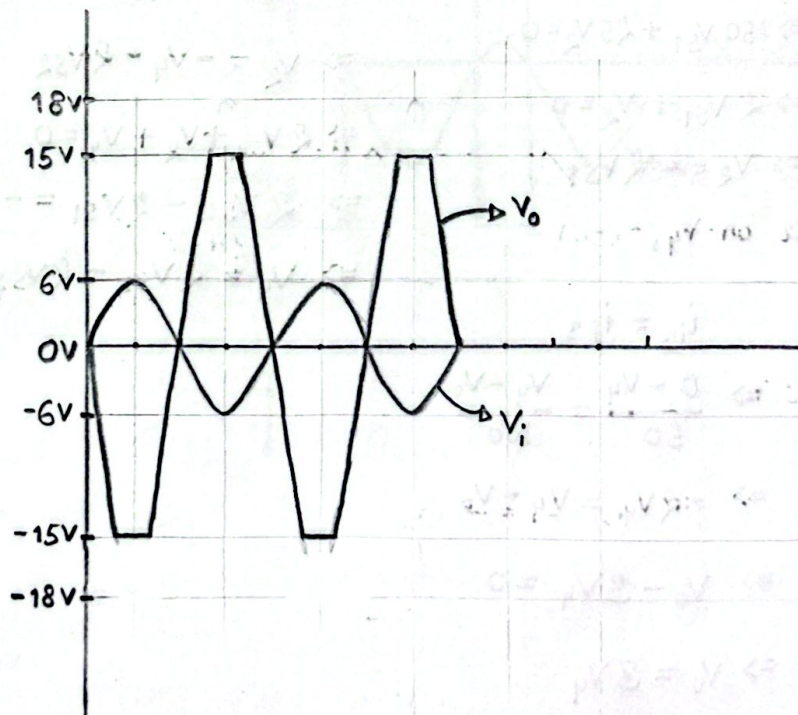

Answer to the Question No-3

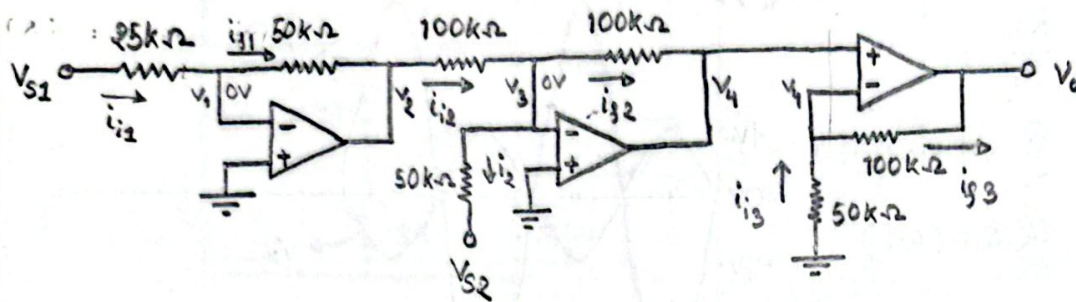KCL on V_1 ,


$$\begin{aligned}
 i_{i1} &= i_{i1} \\
 \Rightarrow \frac{V_{S1} - 0}{25} &= \frac{0 - V_2}{50} \\
 \Rightarrow 50V_{S1} + 25V_2 &= 0 \\
 \Rightarrow 2V_{S1} + V_2 &= 0 \\
 \Rightarrow V_2 &= -2V_{S1}
 \end{aligned}$$

KCL on V_4 ,

$$\begin{aligned}
 i_{i3} &= i_{i3} \\
 \Rightarrow \frac{0 - V_4}{50} &= \frac{V_4 - V_0}{100} \\
 \Rightarrow -2V_4 &= V_4 - V_0 \\
 \Rightarrow V_0 - 3V_4 &= 0 \\
 \Rightarrow V_0 &= 3V_4 \\
 \Rightarrow V_0 &= 3(2V_{S1} - 2V_{S2}) \\
 \Rightarrow V_0 &= 6V_{S1} - 6V_{S2} \\
 \therefore V_0 &= 6(V_{S1} - V_{S2})
 \end{aligned}$$

KCL on V_3 ,

$$\begin{aligned}
 i_{i2} &= i_{i2} + i_{i2} \\
 \Rightarrow \frac{V_2 - 0}{100} &= \frac{0 - V_4}{100} + \frac{0 - V_{S2}}{50} \\
 \Rightarrow V_2 &= -V_4 - 2V_{S2} \\
 \Rightarrow 2V_{S2} + V_2 + V_4 &= 0 \\
 \Rightarrow 2V_{S2} - 2V_{S1} &= -V_4 \\
 \Rightarrow V_4 &= 2V_{S1} - 2V_{S2}
 \end{aligned}$$

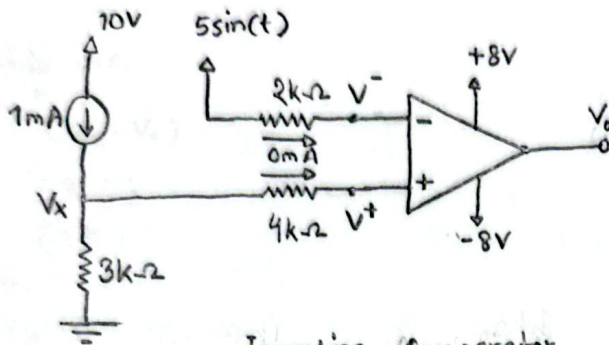Answer to the Question No-4

$$10\text{V (P-P) sine wave} = 5 \sin(t)$$

Inverting Comparator

KCL on V_x ,

$$1 = \frac{V_x - 0}{3}$$


$$\Rightarrow \boxed{V_x = 3\text{V}}$$

Here,

$$V_{\text{ref}} = V^+ = V_x = 3\text{V}$$

$$V_{\text{in}} = V^- = 5 \sin(t)$$

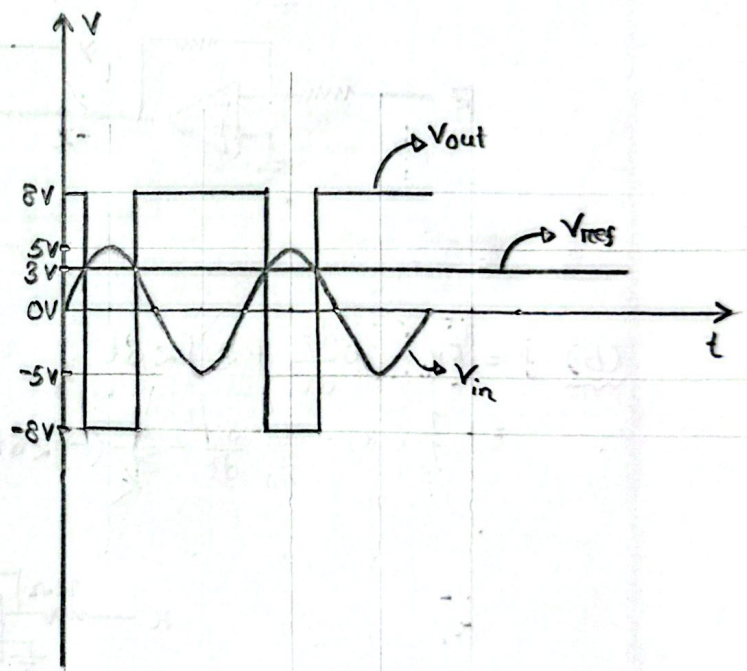
$$V_o = \begin{cases} 8\text{V} & ; V_{\text{in}} < V_{\text{ref}} \\ -8\text{V} & ; V_{\text{in}} > V_{\text{ref}} \end{cases}$$



Answer to the Question No-5

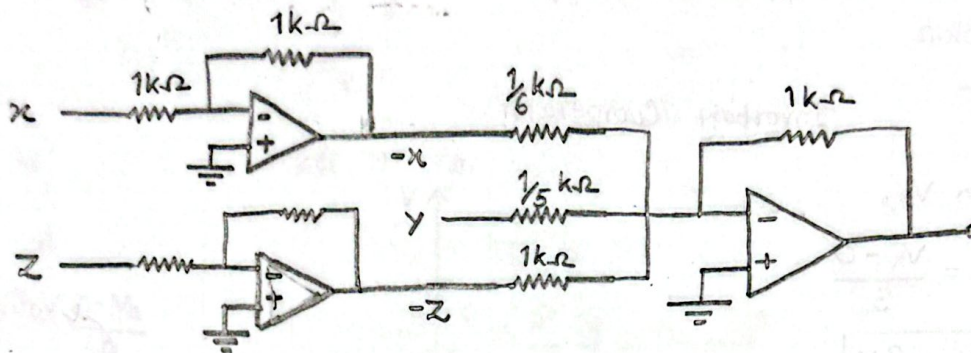
(a) $f = 6x - 5y + z$

$$= -\frac{1}{\frac{1}{6}}(-x) - \frac{1}{\frac{1}{5}}y - \frac{1}{1}(-z)$$



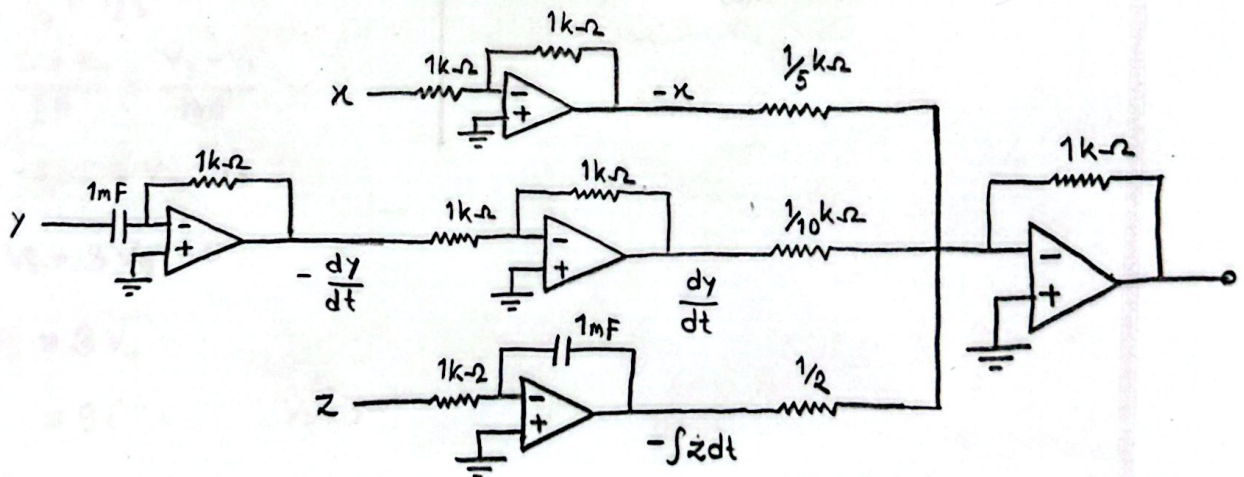(b) $f = 5x - 10 \frac{dy}{dt} + 2 \int z dt$

$$= -\frac{1}{\frac{1}{5}}(-x) - \frac{1}{\frac{1}{10}} \frac{dy}{dt} - \frac{1}{\frac{1}{2}}(-\int z dt)$$



Answer to the Question No-6

Points are.

(V_{in}, V_o)

$(3, 9)$

$(1, 3)$

Now,

$$\frac{V_{in} - 3}{3 - 1} = \frac{V_o - 9}{9 - 3}$$

$$\Rightarrow 2V_o - 18 = 6V_{in} - 18$$

$$\Rightarrow 2V_o = 6V_{in}$$

$$\Rightarrow V_o = \frac{6}{2} V_{in}$$

$$\Rightarrow V_o = 3V_{in}$$


$$\therefore V_o = (1+2)V_{in}$$

Here, gain = (3)


$$\Rightarrow 1 + \frac{R_f}{R_1} = 1 + 2$$


$$\Rightarrow \frac{R_f}{R_1} = 2$$
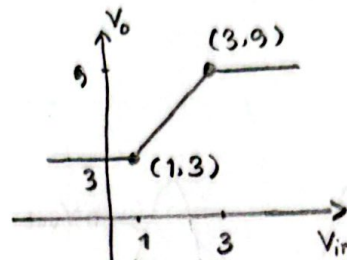
$$\text{Let, } R_f = 2k\Omega \text{ \& } R_1 = 1k\Omega$$



Non-Inverting Amplifier.

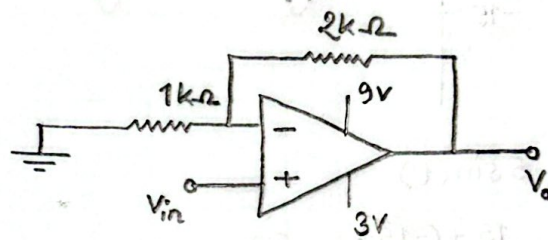

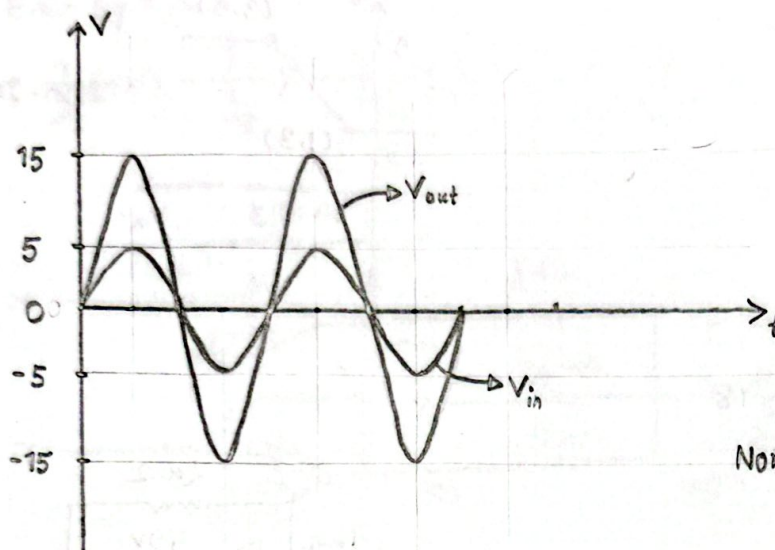Answer to the Question No-7

Non-Inverting

$$V_i = 5 \sin(t)$$


$$\text{gain} = \frac{15 - (-15)}{5 - (-5)} = \frac{30}{10} = 3$$

(i) Using inverting Amplifier.

$$\text{gain} = \frac{R_f}{R_1}$$

$$\Rightarrow 3 = \frac{R_f}{R_1}$$
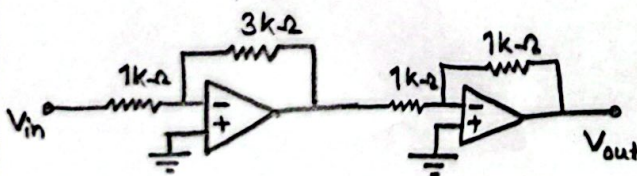
$$\text{let } R_f = 3 \text{ k}\Omega, \text{ \& } R_1 = 1 \text{ k}\Omega$$




(ii) Using Non-Inverting Amplifier


$$\text{gain} = 1 + \frac{R_f}{R_1}$$

$$\Rightarrow 3 = 1 + \frac{R_f}{R_1}$$

$$\Rightarrow \frac{R_f}{R_1} = 2$$
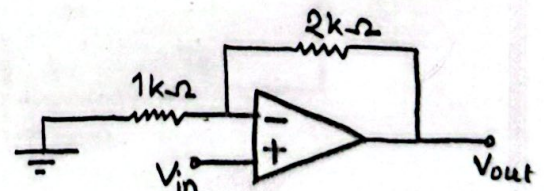
$$\text{let } R_f = 2 \text{ k}\Omega \text{ \& } R_1 = 1 \text{ k}\Omega$$



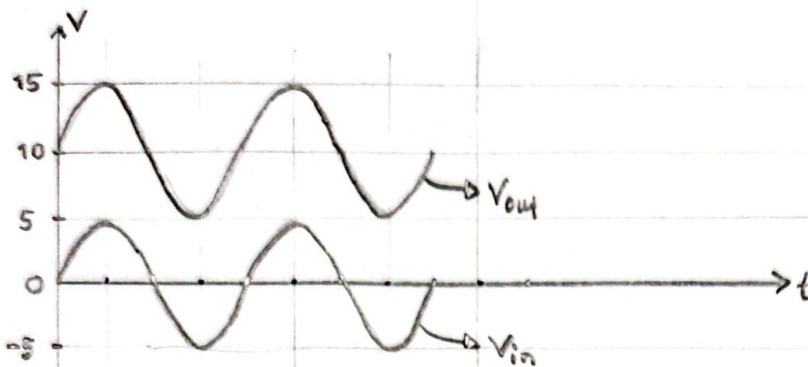Answer to the Question No-8

$$V_{in} = 5 \sin(t)$$

$$V_{out} = 10 + 5 \sin(t)$$

