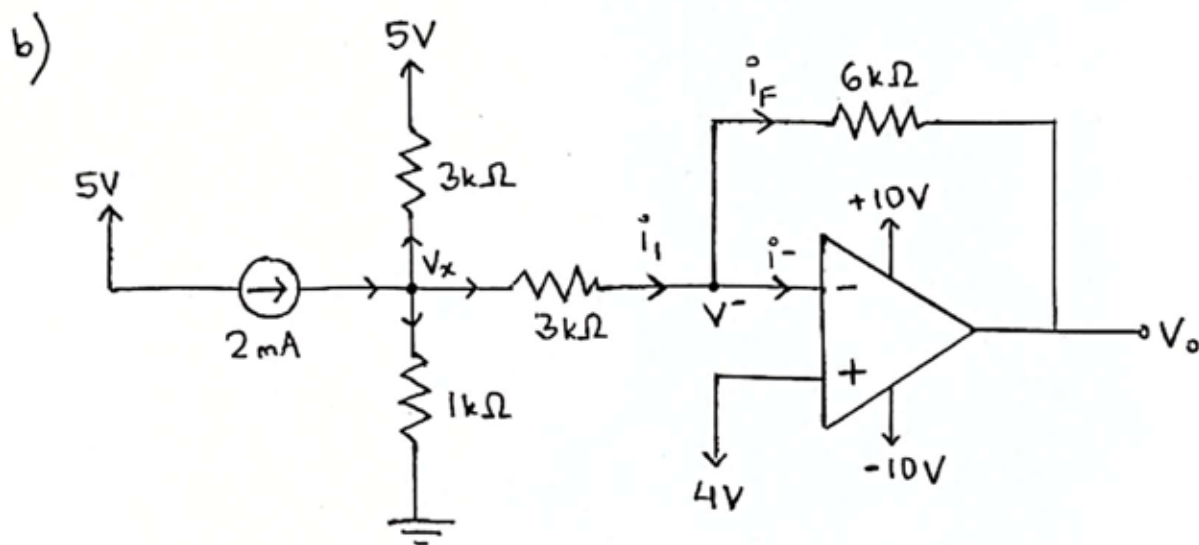


CSE251 Mid Fall 25 (set A)

1) a) $V^- = V^+ = 4V$ (virtual short circuit)



KCL at V_x : $\frac{V_x - 5}{3} + \frac{V_x - V^-}{3} + \frac{V_x}{1} = 2$ [$V^- = 4V$]


$\Rightarrow V_x = 3V$

c) KCL at V^- : $i_1 = i_F + i^-$ [$i^- = 0$]

$\Rightarrow \frac{V_x - V^-}{3} = \frac{V^- - V_o}{6}$

$\Rightarrow V_o = 6V$

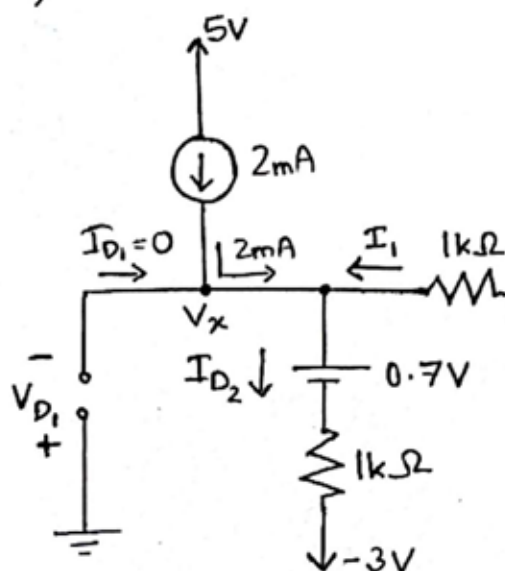2) Reasonable to assume D_1 is OFF and D_2 is ON.



KCL at V_x :

$2 + I_1 = I_{D2}$

$2.3V \Rightarrow 2 + \frac{2.3 - V_x}{1} = \frac{V_x - 0.7 + 3}{1}$

$\Rightarrow V_x = 1V$


Power dissipated in D_2 :

$P_{D2} = I_{D2} \times V_{D2}$
 $= 3.3mA \times 0.7V$
 $= 2.31mW$

For D_1 - $V_{D1} = 0 - 1 = -1 < 0.7V$ (verified)

For D_2 - $I_{D2} = \frac{1 - 0.7 + 3}{1} = 3.3mA > 0$ (verified)

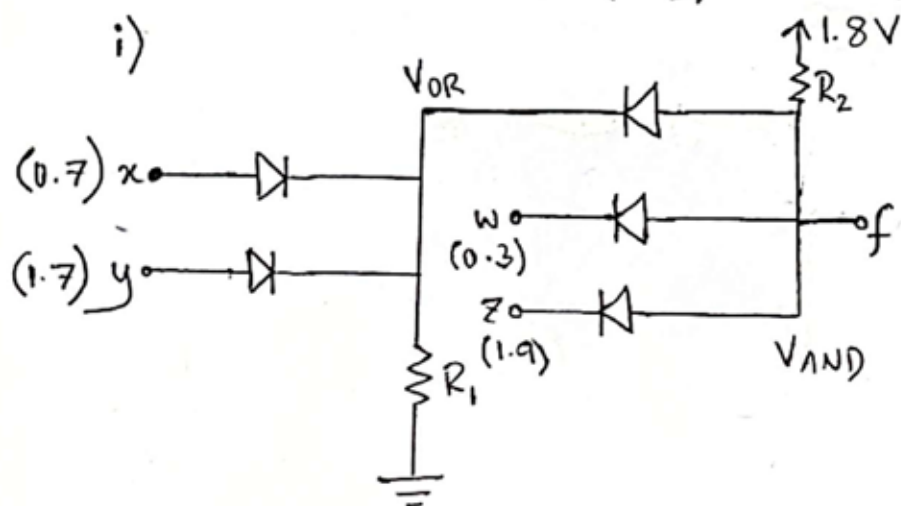3) a) $f = w(x+y)z \rightarrow x+y \rightarrow OR$
 $w \cdot (x+y) \cdot z \rightarrow AND$



ii) $V_{OR} = \max(0.7-0.7, 1.7-0.7)$
 $= 1V$

$V_{AND} = \min(1+0.7, 0.3+0.7, 1.9+0.7)$
 $= 1V$




$\therefore f = 1V$

b) Using graph to find the points where switching occurs will give:

i) $V_{ref} = -4V$

$+V_{sat} = 5V$

$-V_{sat} = 0V$

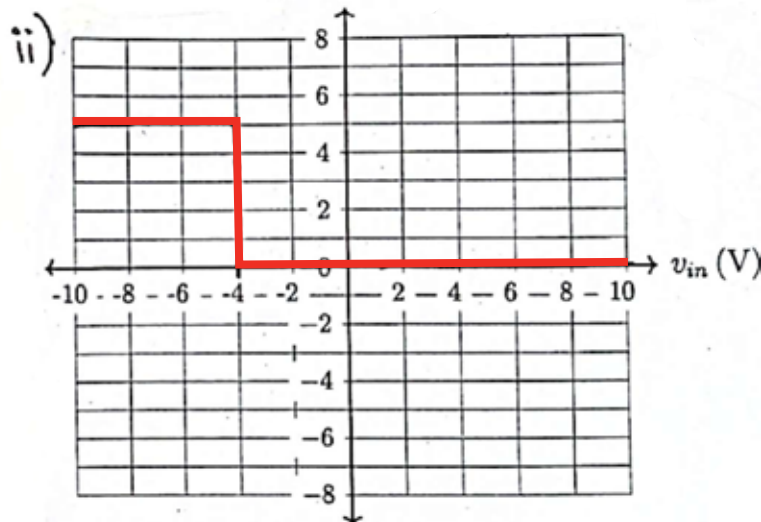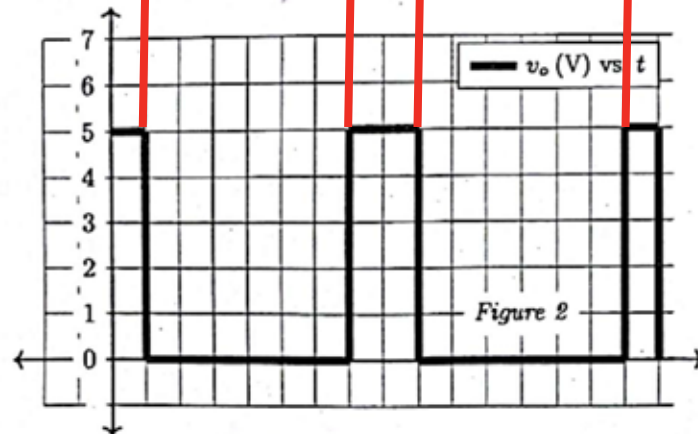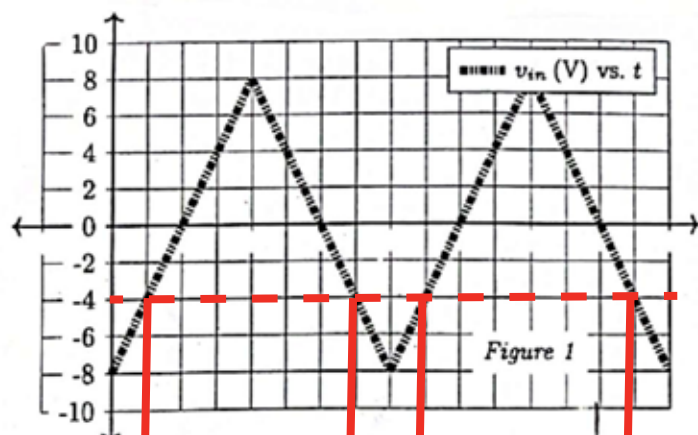

4) a) $z_1 \Rightarrow$ output of ω differentiator

$$z_1 = -RC \frac{dx}{dt}$$

$$= -100 \mu F \times 20 k\Omega \frac{dx}{dt}$$

$$= -2 \frac{dx}{dt}$$

$z_2 \Rightarrow$ output of ω non-inverting amplifier with voltage dividing network at the '+' input (V^+).



$$\text{First, } V^+ = \frac{4}{4+8} \times y = \frac{1}{3} y$$

$$\therefore z_2 = \left(1 + \frac{R_F}{R_1}\right) V^+ = \left(1 + \frac{1}{2}\right) \frac{1}{3} y = \frac{1}{2} y$$

$f \Rightarrow$ output of an inverting summing amplifier with z_1, z_2 as inputs.

$$f = -\frac{1}{1} z_1 - \frac{1}{3} z_2 = +2 \frac{dx}{dt} - \frac{1}{6} y$$

b)

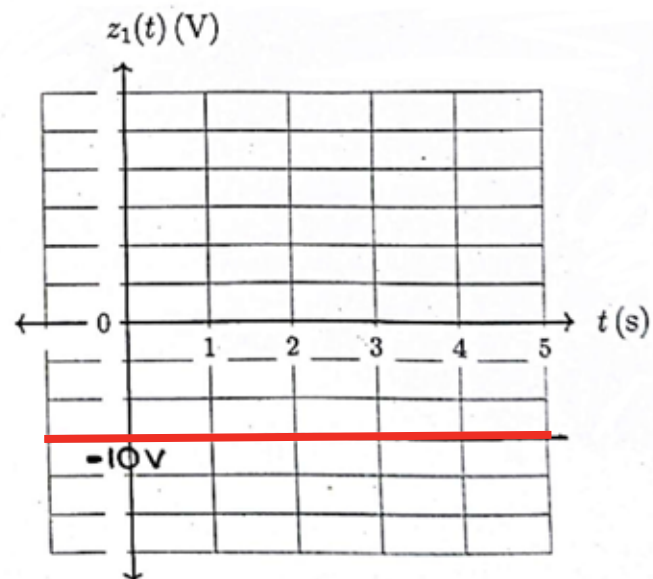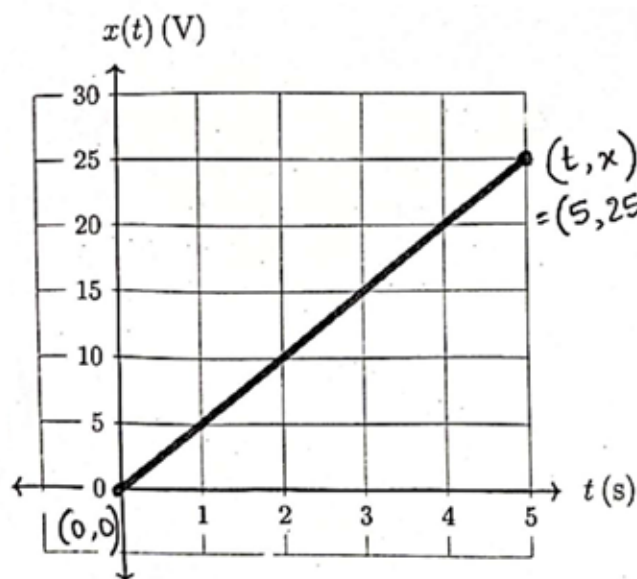

$$\text{slope} = \frac{\Delta x}{\Delta t} = \frac{25-0}{5-0} = 5$$


$$\downarrow$$

$$\frac{\Delta y}{\Delta x}$$



$\therefore$ equation of straight line $\Rightarrow x = 5t$

$$\Rightarrow z_1 = -2 \frac{dx}{dt} = -2 \frac{d}{dt} (5t) = -2 \times 5 = -10$$

5) a) CVD+R model is more accurate.

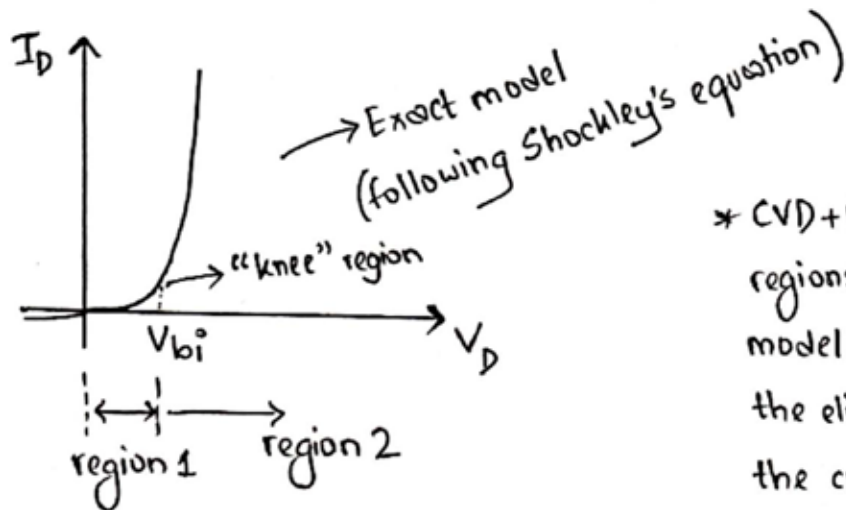

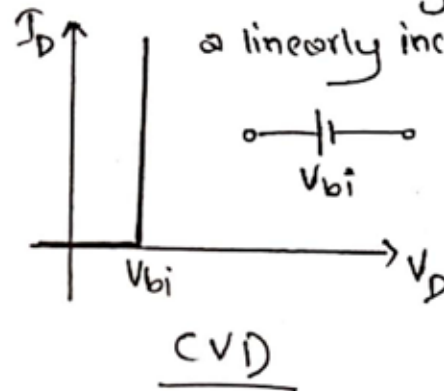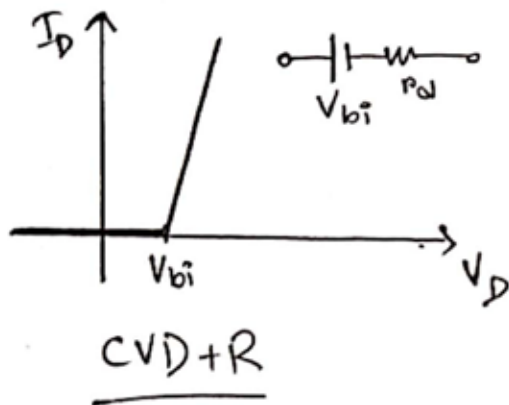* CVD+R model represents both regions 1 and 2 of the exact/real model, with the inaccuracy being the elimination of the "knee" in the curve, and that the exponential increase in region 2 is replaced with a linearly increasing current.



* CVD model further decreases accuracy, as the increase in voltage in region 2 is neglected (as diode resistance is removed).

b) i) correct

ii) False. It is zero only when negative feedback is provided.

iii) correct

c) From left to right: B, D, D, B