

Practice Problem Set 3.3

CSE251 - Electronic Devices and Circuits

DIODE LOGIC CIRCUITS

OR Gate, AND Gate, and Cascaded Logic Circuits

[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)

Problem 1

- Implement the following logic functions using diodes. Here, A , B , C , and D are Boolean inputs. Here “+” and “.” denotes logical OR and AND, respectively.

I. $A.C + B + D$ [Fall 2024]

II. $A.C + B + D$ [Fall 2024]

III. $(A + B).(C + D)$ [Fall 2023]




IV. $(A + B).C + D.E$ [Fall 2025]

V. $A.B.C + D$ [Spring 2025]

VI. $(A + B + C).D$ [Spring 2025]

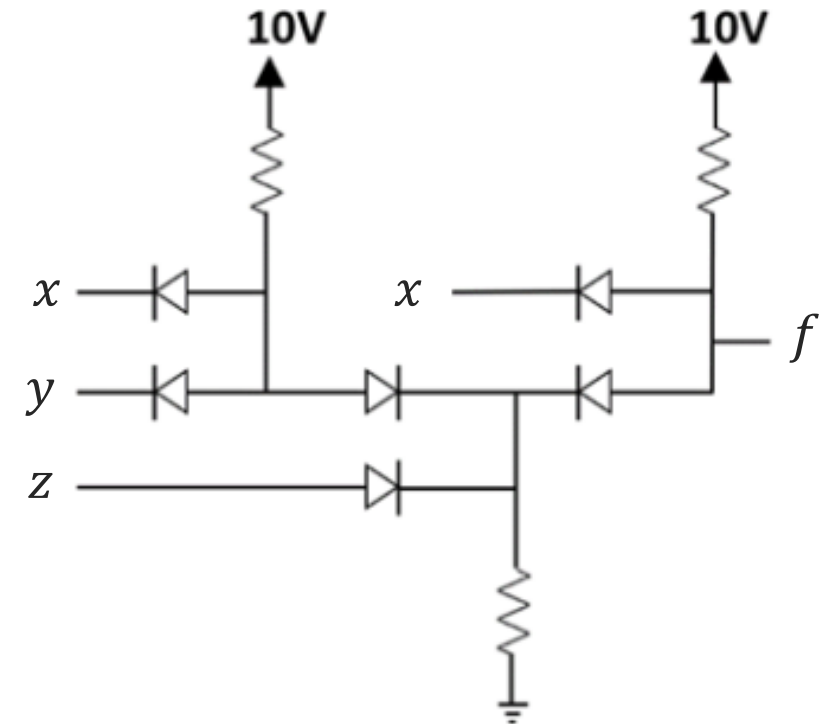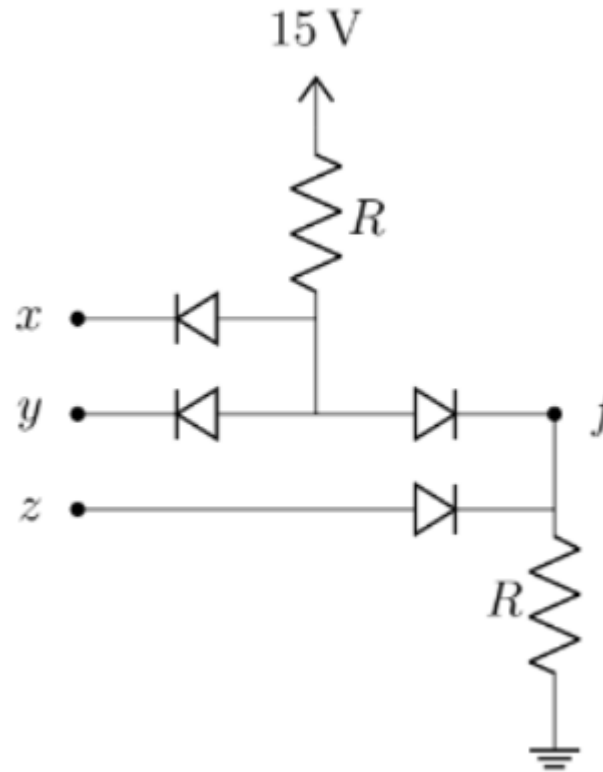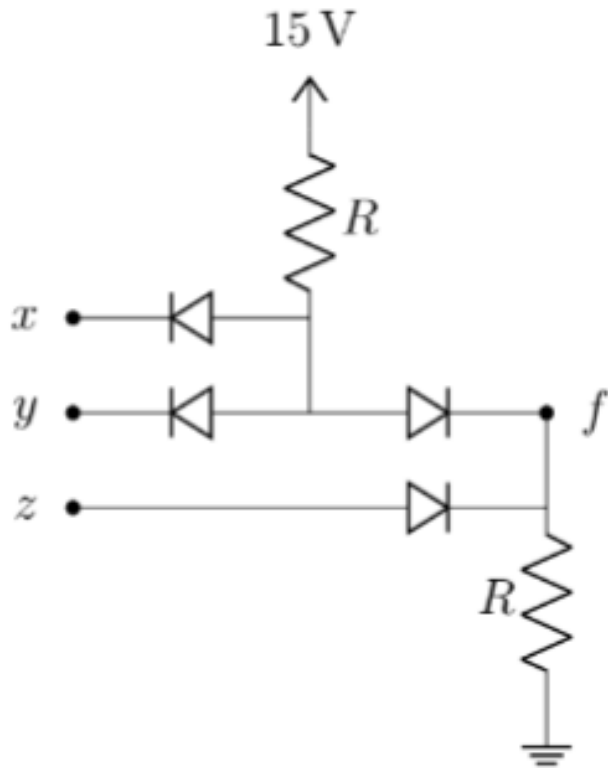
Problem 2

- For each of the circuits shown below, assuming x , y , and z are Boolean inputs, express f in terms of x , y , and z .





100

- 
- BRAC
UNIVERSITY
- Inspiring Excellence

 4

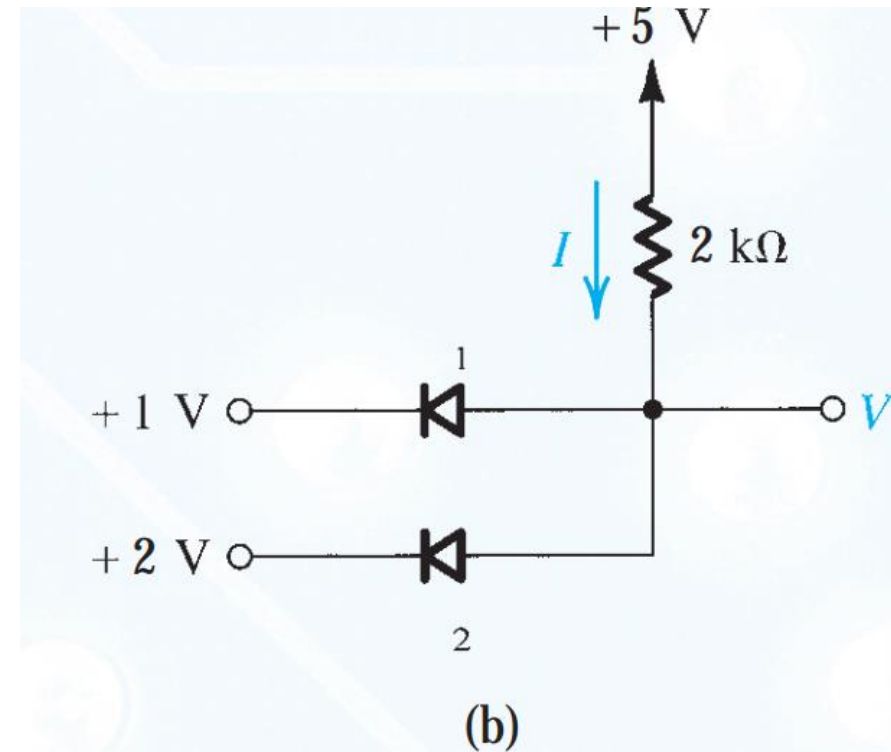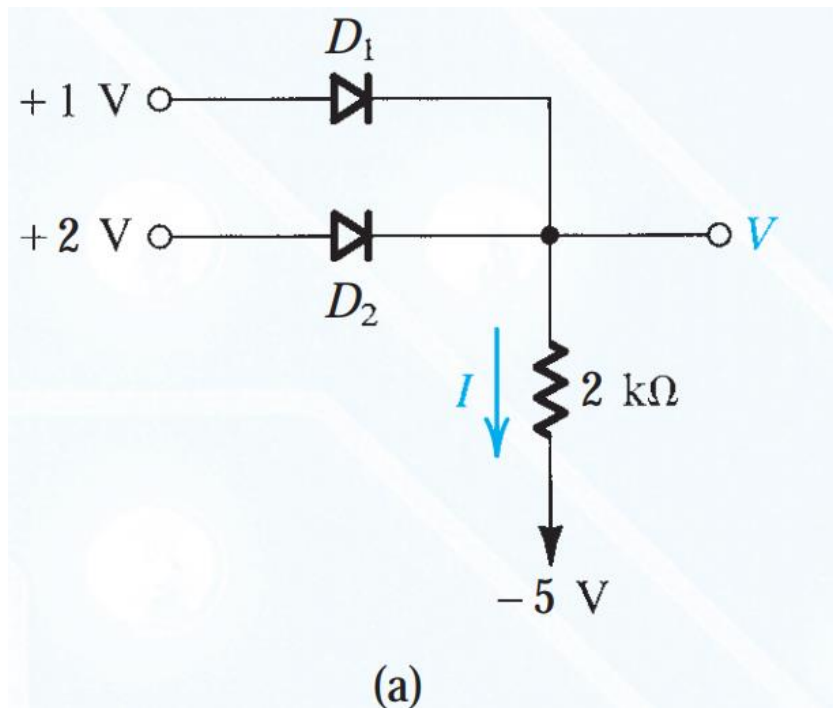Problem 4


- For the logic circuits shown below, use ideal diode model, find the values of the voltages and currents indicated.




Ans: (a) $V = 2\text{ V}$, $I = 2.5\text{ mA}$; (b) $V = 1\text{ V}$, $I = 2\text{ mA}$

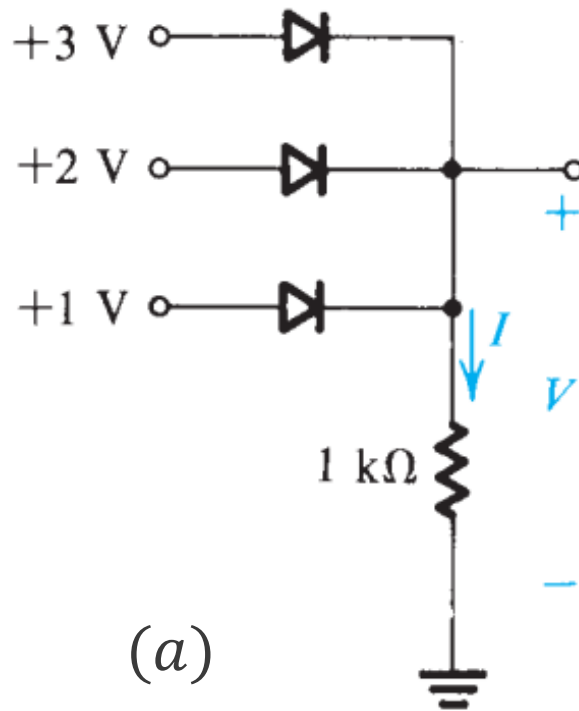Problem 5

- For the logic circuits shown below, use ideal diode model, find the values of the voltages and currents indicated.



(a)

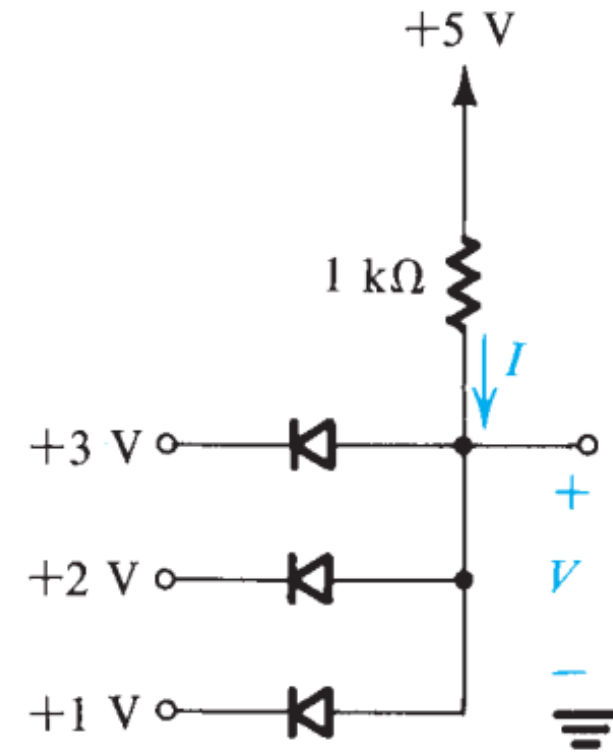


(b)


Ans: (a) $V = 3\text{ V}$, $I = 3\text{ mA}$; (b) $V = 1\text{ V}$, $I = 4\text{ mA}$

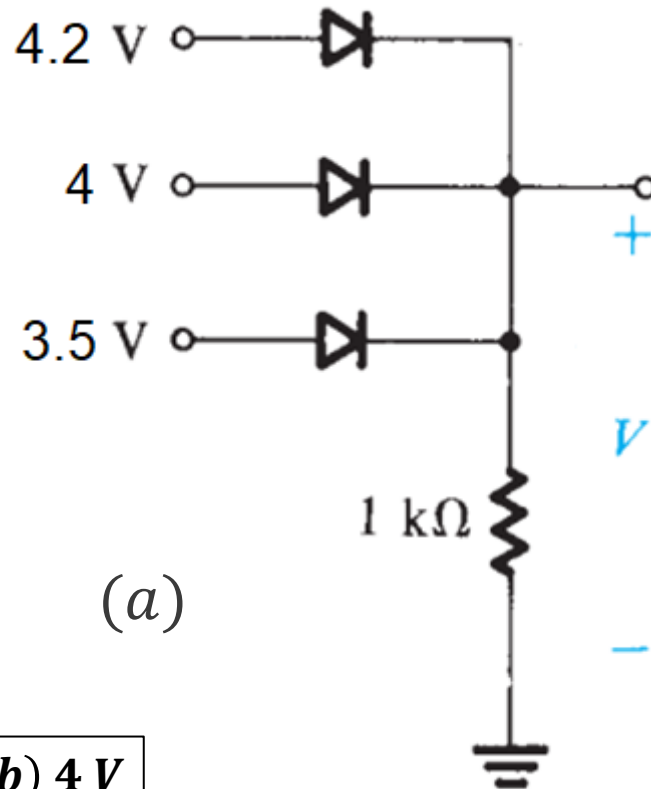Problem 6

- For each of the circuits shown below, use CVD model, find the values of the voltages and currents indicated. Take $V_{D_{o1}} = 1\text{ V}$, $V_{D_{o2}} = 0.7\text{ V}$, and $V_{D_{o3}} = 0.5\text{ V}$.



(a)


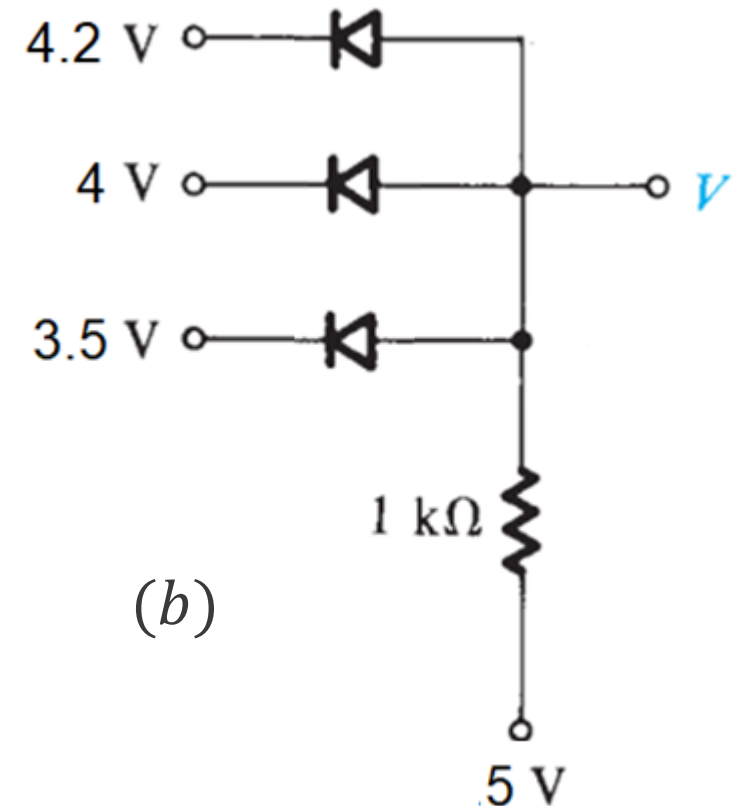


(b)

Ans: (a) $V = 3.3\text{ V}$; (b) 4 V

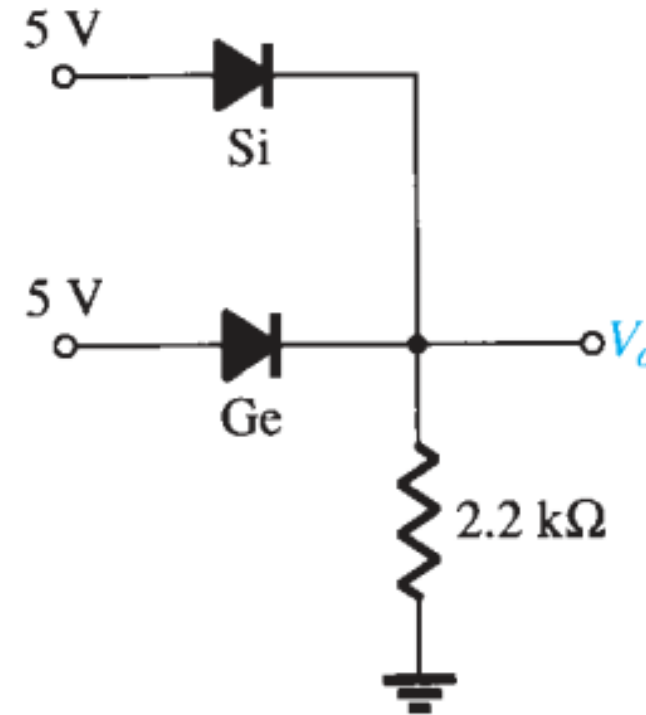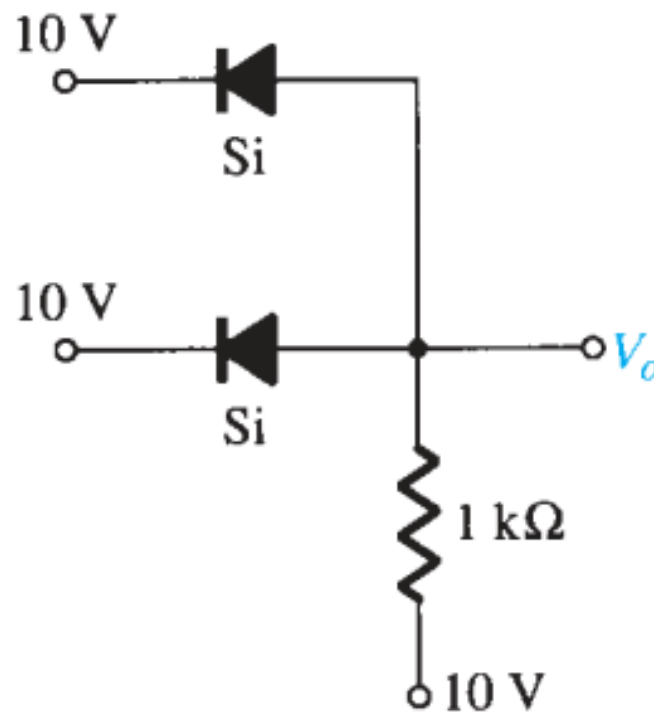Problem 7


- For the logic circuits shown below, determine. Use CVD+R model with $V_{D_o, Si} = 0.7\text{ V}$ and $V_{D_o, Ge} = 0.3\text{ V}$ and $r_o = 10\ \Omega$ for both.



Ans: (a) $V_o = 10.7\text{ V}$; (b) $V_o = 4.7\text{ V}$

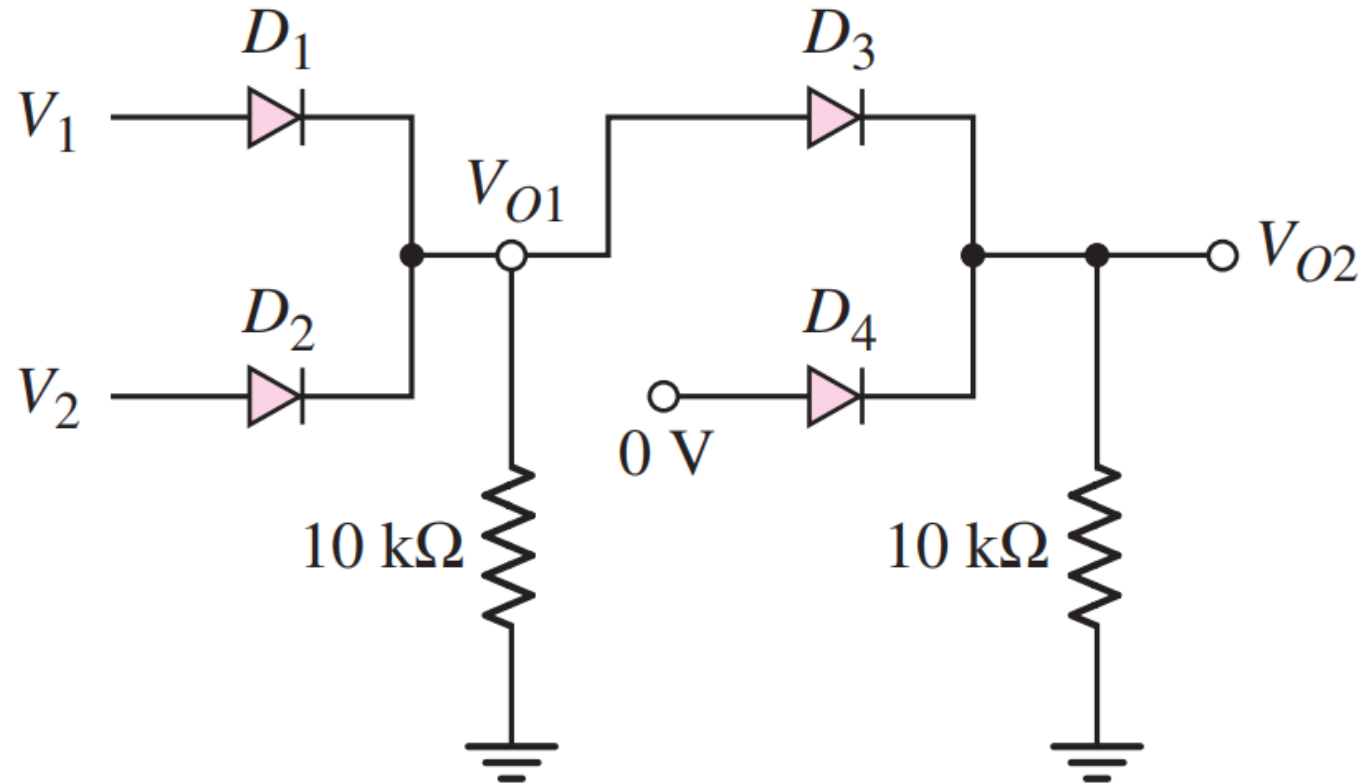Problem 8


- From the logic network shown, express V_{O2} as a Boolean expression of V_1 and V_2 . Determine V_{O2} if $V_1 = 3\text{ V}$ and $V_2 = 1\text{ V}$. Use CVD model with $V_{D_o} = 0.7\text{ V}$.



Ans: $V_{O2} = 2\text{ V}$

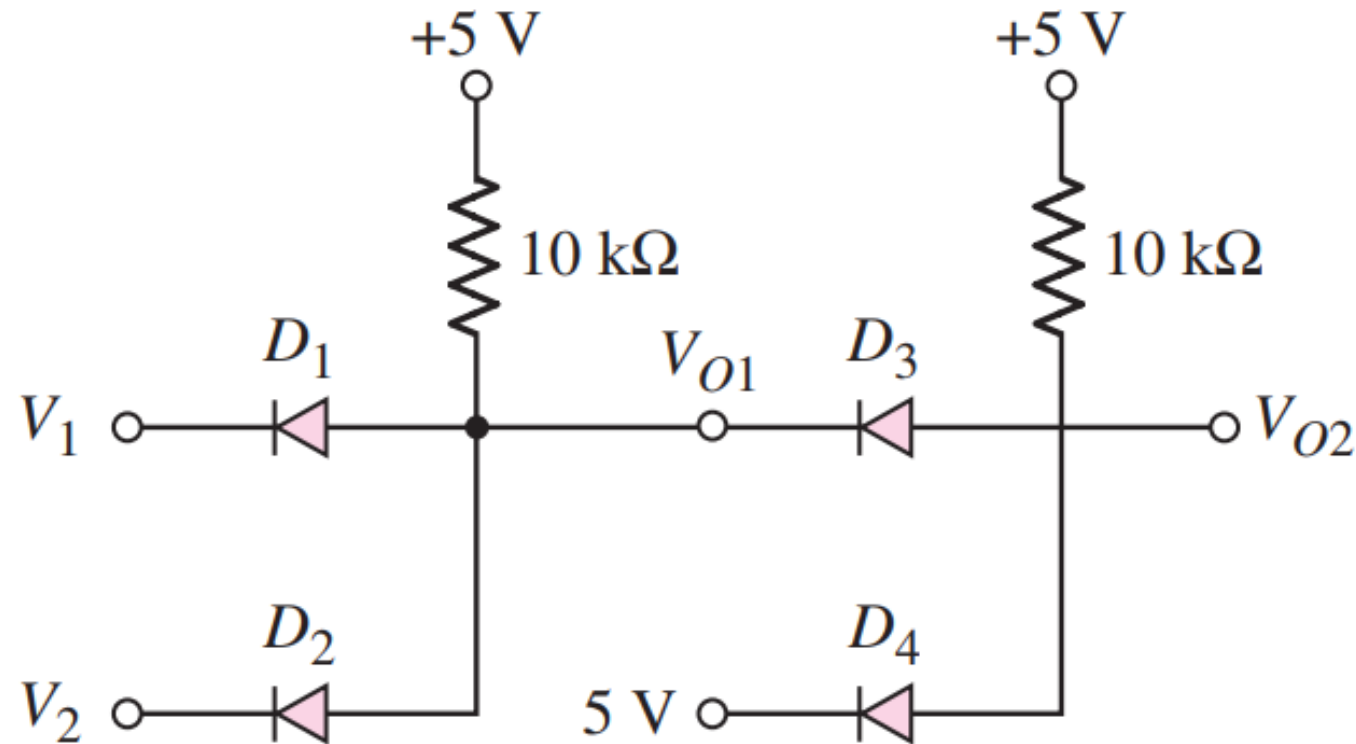Problem 9


- From the logic network shown, express V_{O2} as a Boolean expression of V_1 and V_2 . Determine V_{O2} if $V_1 = 3\text{ V}$ and $V_2 = 1\text{ V}$. Use CVD model with $V_{D_o} = 0.7\text{ V}$.



Ans: $V_{O2} = 2.4\text{ V}$

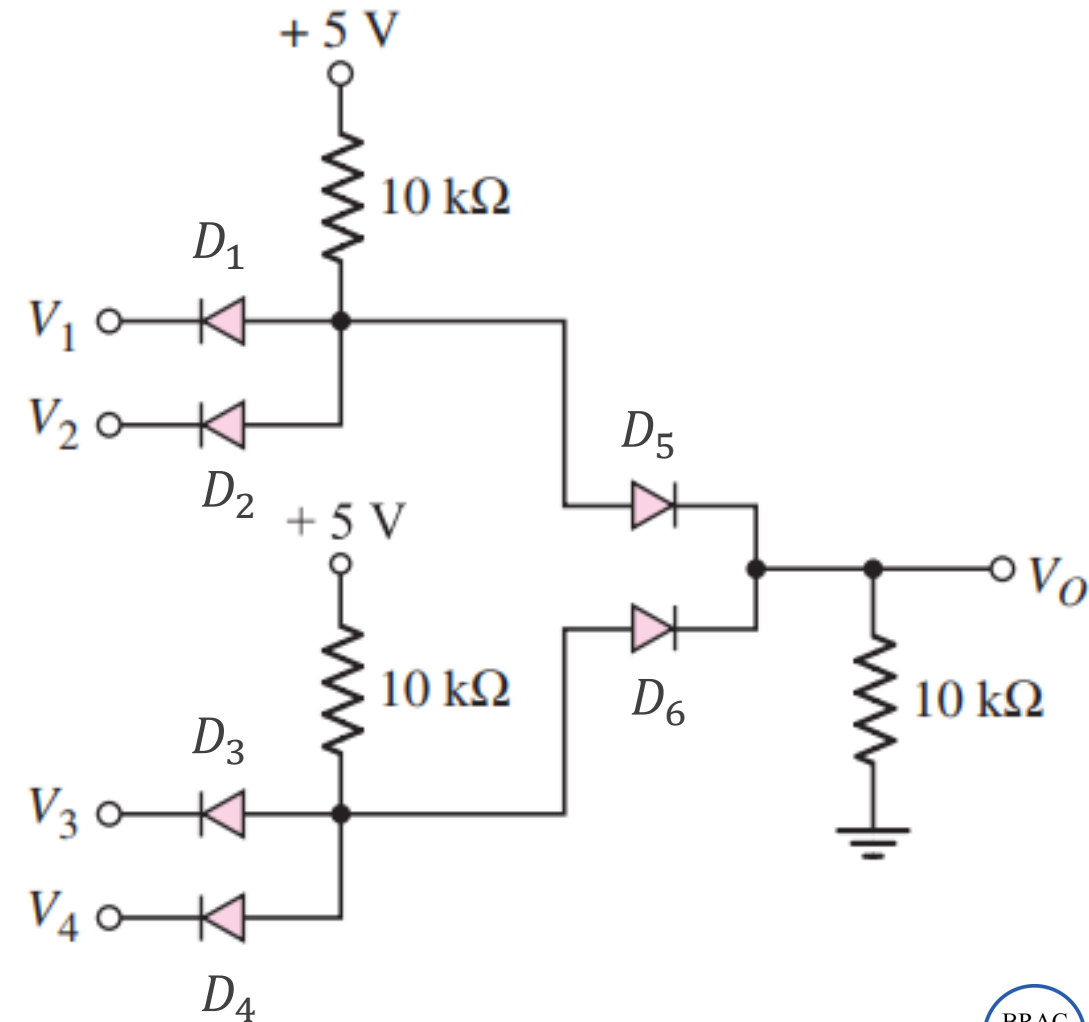Problem 10

- From the logic network shown, determine V_O if $V_1 = 2\text{ V}$, $V_2 = 2.2\text{ V}$, $V_3 = 2.4\text{ V}$, and $V_4 = 2.5\text{ V}$. Use CVD model with $V_{D_{o1}} = 0.3\text{ V}$, $V_{D_{o2}} = 0.5\text{ V}$, $V_{D_{o3}} = 0.7\text{ V}$, $V_{D_{o4}} = 0.9\text{ V}$, $V_{D_{o5}} = 1\text{ V}$, and $V_{D_{o6}} = 1.5\text{ V}$.



Ans: $V_O = 1.6\text{ V}$

Up Next

Relevant *Questions* from Past Semesters

Mid — Fall 2025

In a diode logic circuit, a logic HIGH is approximately 1.8 V , while a logic LOW is approximately 0 V . The circuit is designed to implement the Boolean function

$$f = w \cdot (x + y) \cdot z,$$

where, w , x , y , and z are the Boolean inputs and f is the Boolean output.

- Draw the diode logic circuit that realizes the Boolean function given above.
- For this logic circuit, determine the output voltage corresponding to the input values $w = 0.3\text{ V}$, $x = 0.7\text{ V}$, $y = 1.7\text{ V}$, and $z = 1.9\text{ V}$. Assume all diodes are identical with negligible resistance and have a cut-in voltage of 0.7 V .

Ans: (b) $f = 1\text{ V}$



Inspiring Excellence



Mid — Summer 2025

If x , y , and z are Boolean inputs and f is the output,

- a. Design a circuit using diode logic to implement the following Boolean function:

$$f = x.y + z$$

- b. Given the input voltages $x = 3.3\text{ V}$, $y = 3.0\text{ V}$, and $z = 2.7\text{ V}$, determine the output voltage of the logic circuit designed in (a). Assume a supply voltage of 5 V , where applicable. Also, assume that the diodes have a cut-in voltage of $V_{D_0} = 0.7\text{ V}$ and negligible resistance compared to other components.

Ans: (b) $f = 3\text{ V}$




Inspiring Excellence



Mid — Spring 2025

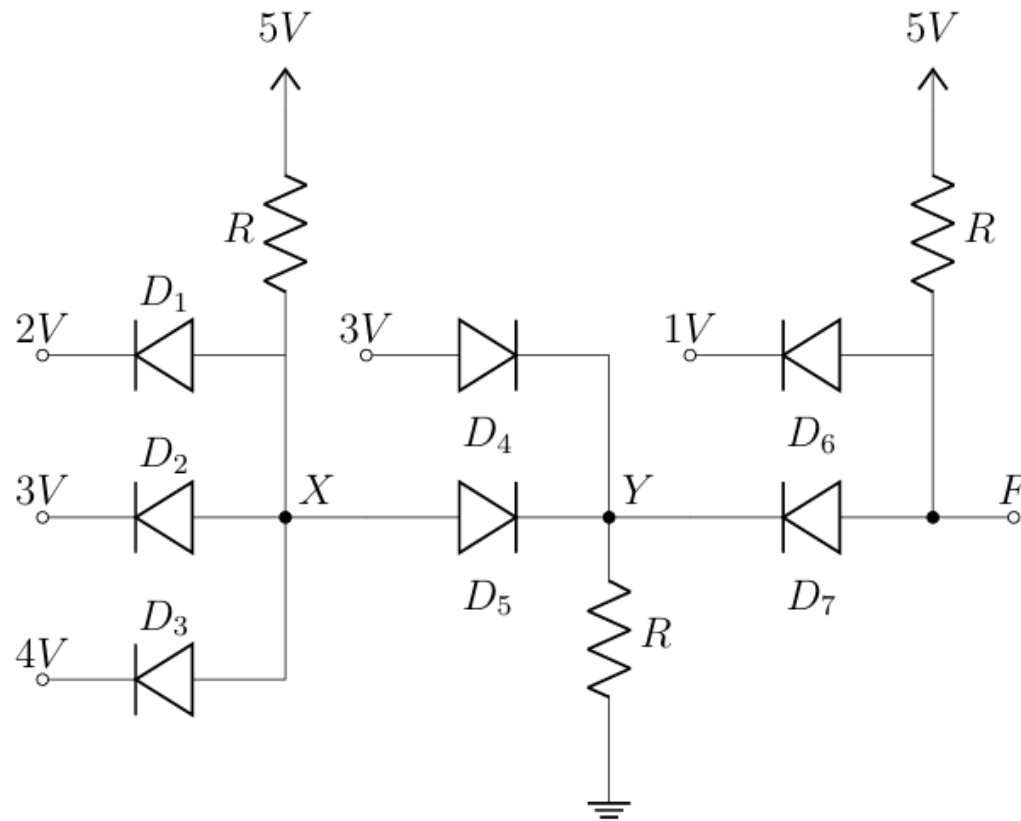
- Assuming that all the diodes are ideal on the following circuit, determine V_F .



Ans: $V_F = 1V$

Mid — Fall 2024

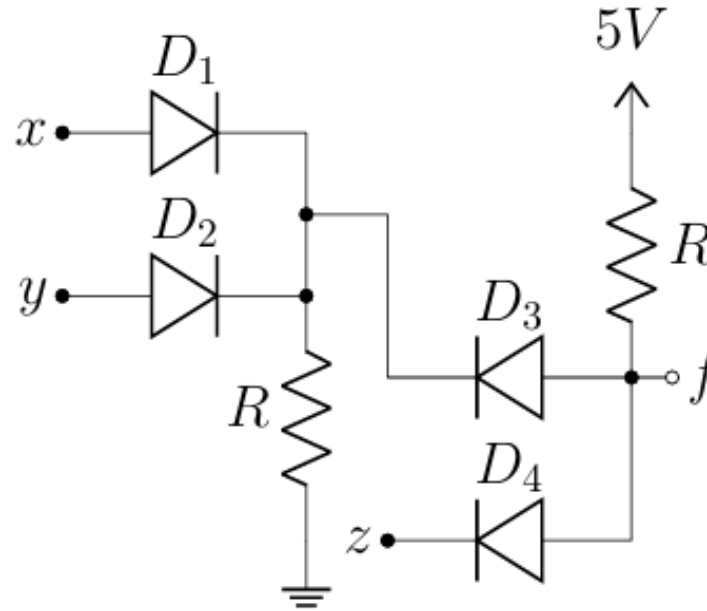- If x , y , and z are the Boolean inputs and f is the Boolean output, for the logic circuit shown below, write an expression for f .




$$\text{Ans: } f = (x + y) \cdot z$$

Mid — Summer 2024

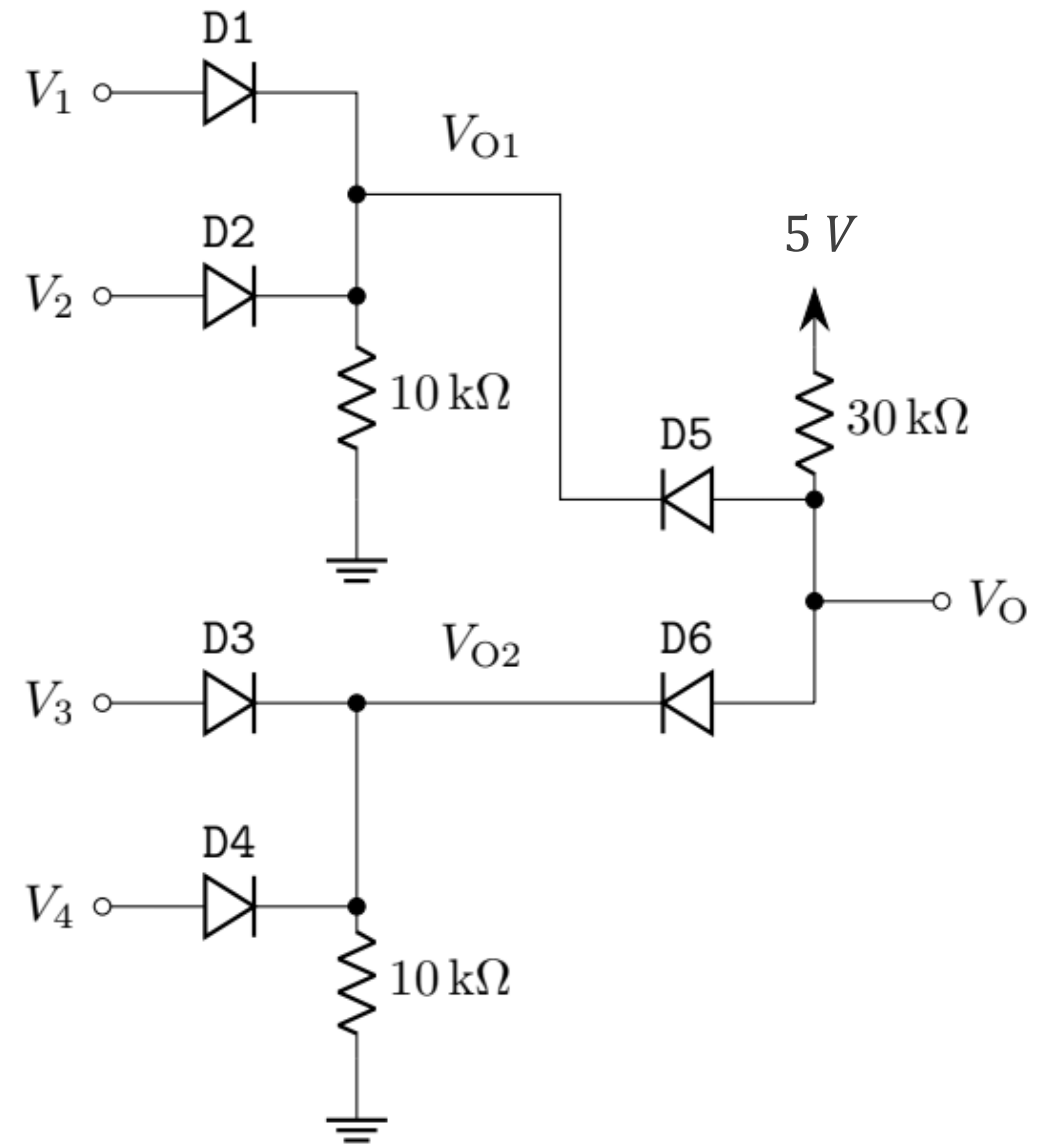- a. From the logic network shown, determine V_{O1} , V_{O2} , and V_O if $V_1 = 2\text{ V}$, $V_2 = 2.2\text{ V}$, $V_3 = 2.4\text{ V}$, and $V_4 = 2.5\text{ V}$. Use CVD model with $V_{D_{o1}} = 0.3\text{ V}$, $V_{D_{o2}} = 0.7\text{ V}$, $V_{D_{o3}} = 0.5\text{ V}$, $V_{D_{o4}} = 0.9\text{ V}$, and $V_{D_{o5}} = V_{D_{o6}} = 1\text{ V}$.
- b. Now if V_3 and V_4 are changed to -2 V and -3 V while keeping all other parameters unchanged, identify the states of the diodes D_3 and D_4 . Determine V_O .


[Hint: V_{O2} cannot be calculated as in (a) for negative V_3 and V_4 . You need to apply method of assumed states to check the states of D_5 and D_6 .]



Ans: (a) $V_{O1} = 1.7\text{ V}$, $V_{O2} = 1.9\text{ V}$, $V_O = 2.7\text{ V}$; (b) $V_{O1} = 1.7\text{ V}$, $D_5 \rightarrow \text{OFF}$, $D_6 \rightarrow \text{ON}$, $I_{D_6} = 0.1\text{ mA}$, $V_{D_5} = 0.3\text{ V}$, $V_O = 2\text{ V}$

Mid — Summer 2023

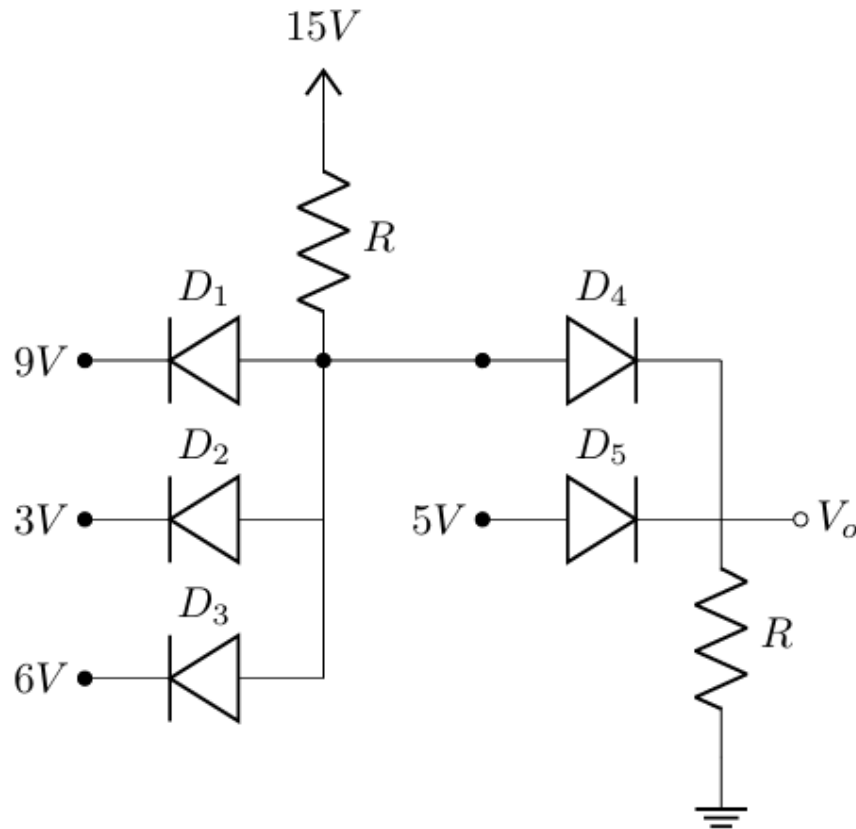
- Assuming all the diodes in the following logic circuit are ideal, determine V_o .



Ans: $V_o = 5V$

Mid — Spring 2023



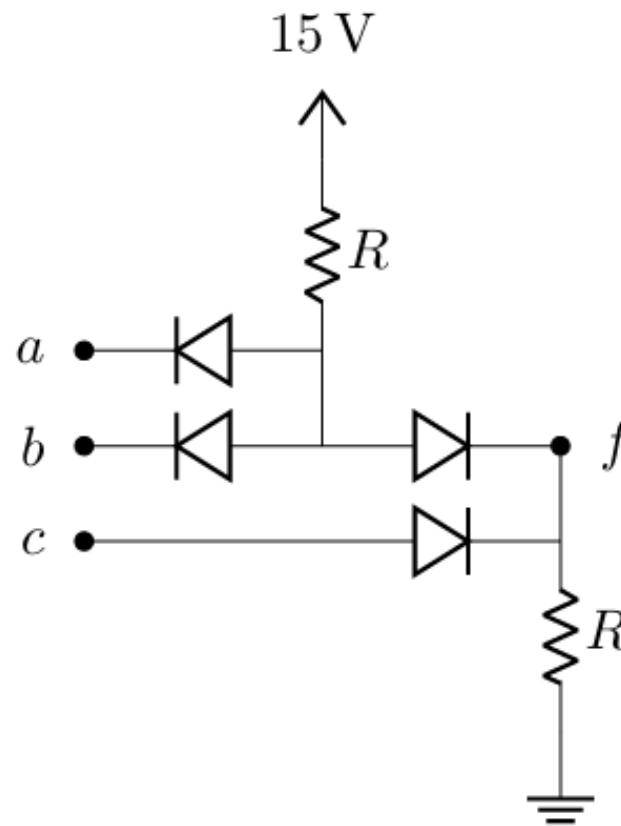
- If a , b , and c are the Boolean inputs and f is the Boolean output, for the logic circuit shown below, write an expression for f in terms of the inputs.



$$\text{Ans: } f = a \cdot b + c$$

Mid — Fall 2022

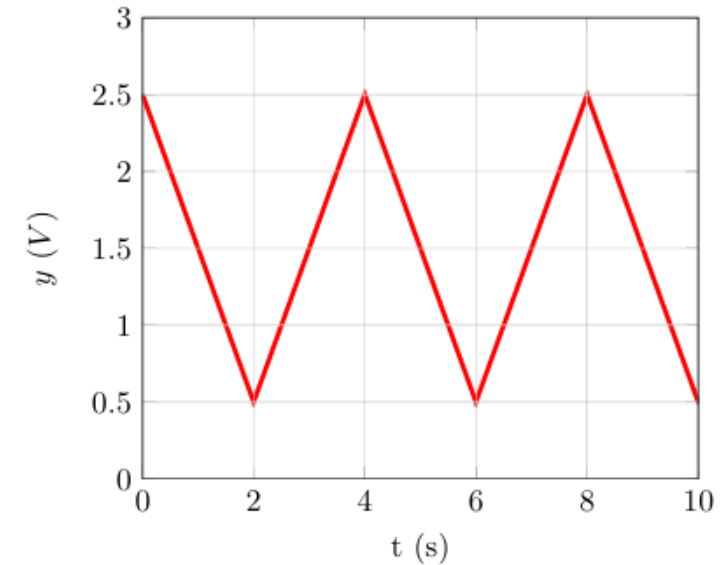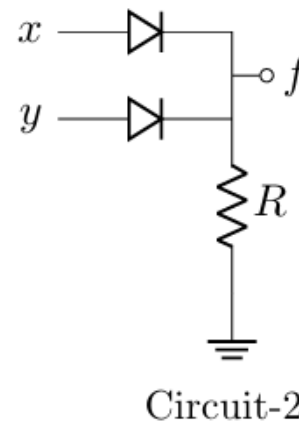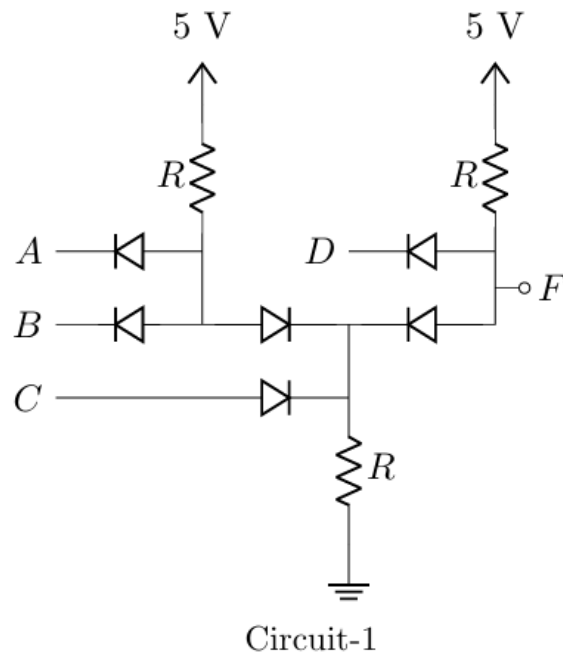
- If A , B , C , and D are the Boolean inputs and F is the Boolean output, for the Circuit-1, write an expression for F .
- Draw a voltage vs. time graph for the voltage at f assuming x and y are voltage signals, where $x = 1.5\text{ V}$ and y has a waveform as shown in the Graph-1.



$$\text{Ans: (a) } F = (A \cdot B + C) \cdot D$$

Mid — Summer 2022

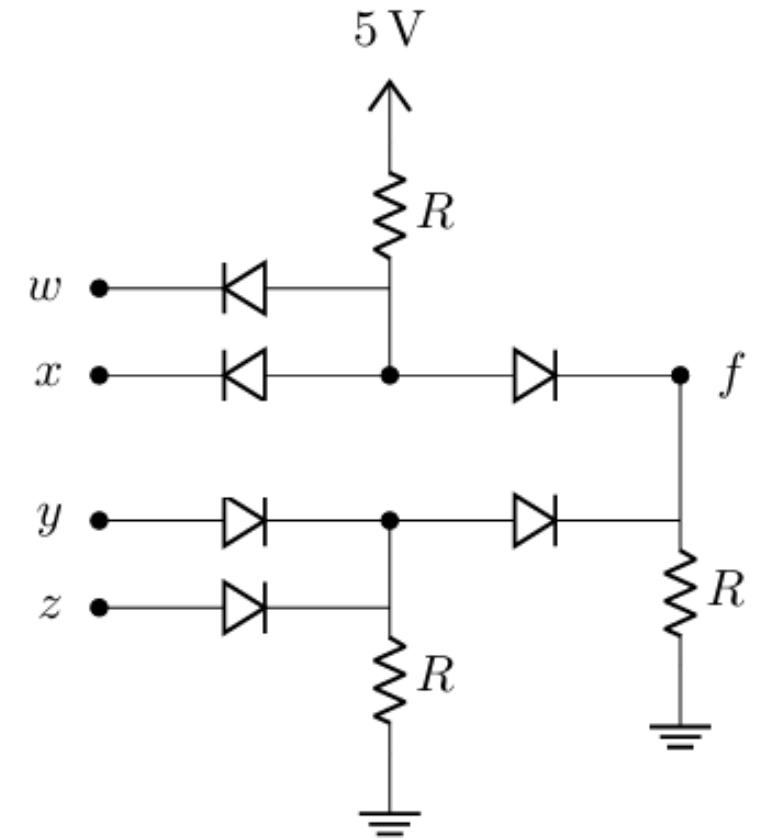- a. If w , x , y , and z are the Boolean inputs and f is the Boolean output, for the logic circuit shown below, write an expression for f in terms of the inputs.
- b. Jawad has created a new ride sharing app- *Juber*. When you request a Juber ride, Juber's algorithm generates 4 signals to determine whether it will be forwarded to a rider. (1) Signal F determines if the rider is free. (2) Signal R determines if the rider is within close proximity. (3) Signal G determines if the rider has good rating. (4) Signal N determines if the rider is new. If both conditions 1 and 2 are satisfied, and either condition 3 or condition 4 are satisfied, the request will be connected.
- Deduce the logic function using the Boolean signals F , R , G , and N to implement the Juber's algorithm.
 - Design a circuit using ideal diode logic gates to implement this function derived in (i).



$$\text{Ans: } (a) f = w \cdot x + y \cdot z$$

Acknowledgement and References

Some of the problems in this set are taken or adapted from the following sources:

1. Sedra, A. S., & Smith, K. C., Microelectronic Circuits, Oxford University Press
2. Neamen, D. A., Microelectronics: Circuit Analysis and Design, McGraw-Hill