

Practice Problem Set 6

CSE251 – Electronic Devices and Circuits

BJT CIRCUITS

Logic Function Implementation, Modes of Operation, Method of Assumed States, Multistage Circuits, MOSFET-BJT Hybrid Problems

I_B , I_C , and I_E denote the base, collector, and emitter currents, respectively. Similarly, V_B , V_C , and V_E denote the corresponding voltages. “Sat” and “Active” refer to the saturation and active regions, respectively. k_n and k'_n denote MOSFET’s transconductance and process transconductance parameters, respectively. V_{Tn} denote the threshold voltage of the MOSFETs. β denote the common emitter current gain of BJTs.

[Course Description, COs,
and Policies](#)



[Midterm and Final
Questions](#)

Problem 1

- Give a switch-BJT implementation of the following logic functions. A , B , C , D , E and F are the Boolean inputs and f is the Boolean output. Here, "+" and "." represent the logical *OR* and *AND* operations, respectively.

$$I. \quad f = A.\bar{B}$$

$$II. \quad f = \overline{A.B.C + D.E}$$

$$III. \quad f = \overline{A + B.C + D} \quad \text{[Summer 2024]}$$

$$IV. \quad f = A.B + \bar{A}.\bar{B} \quad \text{[Fall 2024]}$$

$$V. \quad f = \overline{A.C} + \overline{B + C}$$

$$VI. \quad f = (A.B + C).D$$

$$VII. \quad f = A.B + B.C + C.A$$

$$VIII. \quad f = (A + B).(C + D)$$

$$IX. \quad f = (A + B).C + D.E$$

$$X. \quad f = \bar{A}.B + \bar{B}.A + \bar{C}.A \quad \text{[Spring 2025]}$$

$$XI. \quad f = (A.B + C).D.(E + F)$$


$$XII. \quad f = A \oplus B$$

$$XIII. \quad f = \overline{(A + B + C).D + \bar{D}}$$

$$XIV. \quad f = \overline{C.(A + B)}.(A + \bar{B} + C)$$

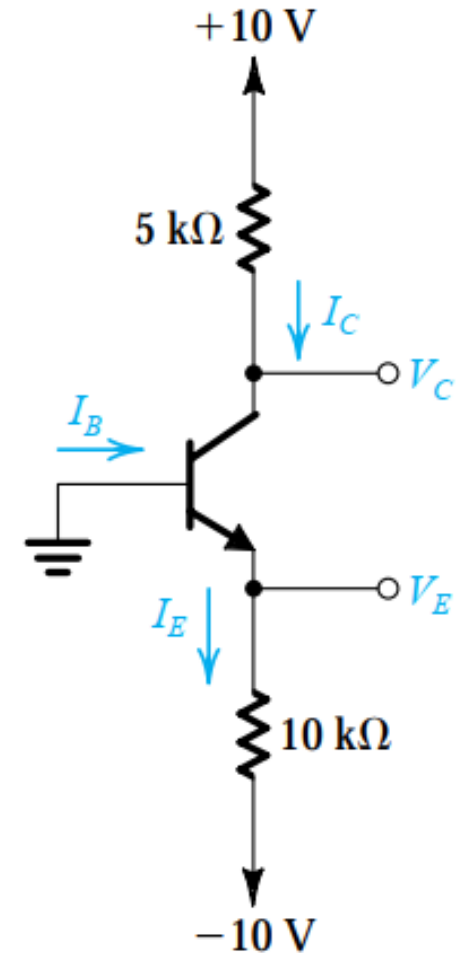Problem 2


- For the adjacent circuit, V_E was measured and found to be -0.7 V . If $\beta = 50$, determine I_E , I_B , I_C , and V_C .




Ans: **Active**; $I_E = 0.93\text{ mA}$; $I_B = 18\text{ }\mu\text{A}$; $I_C = 0.91\text{ mA}$; $V_C = 5.45\text{ V}$; $V_E = -0.7\text{ V}$

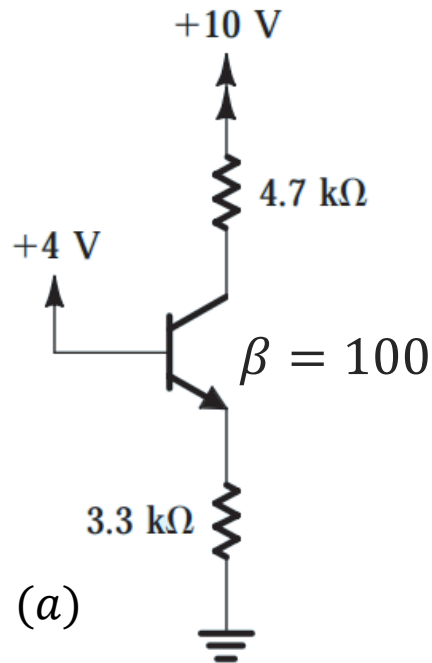Problem 3


- Determine and verify the operating region for each of the transistors in the following circuits. Assume $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$.



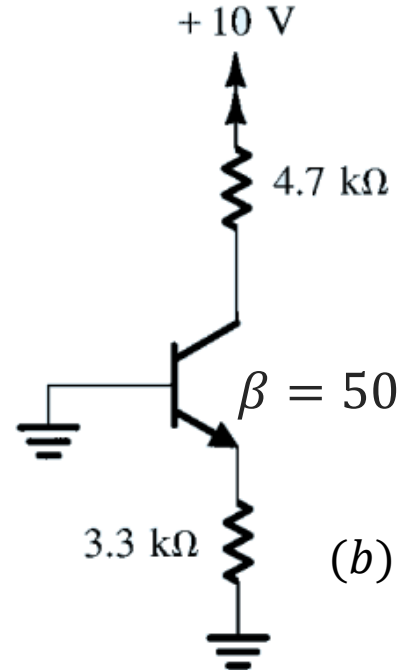Ans: **Active**; $I_C = 0.99\text{ mA}$; $I_E = 1\text{ mA}$; $I_B = 10\text{ }\mu\text{A}$; $V_B = 0\text{ V}$; $V_C = 5.347\text{ V}$; $V_E = 3.3\text{ V}$



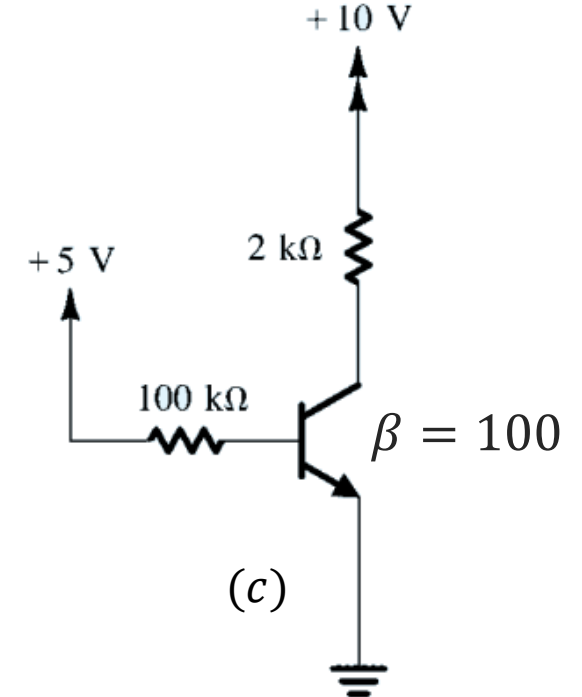
Ans: **Cutoff**; $I_C = I_E = I_B = 0$; $V_B = V_E = 0\text{ V}$; $V_C = 10\text{ V}$




Ans: **Active**; $I_C = 4.3\text{ mA}$; $I_E = 4.343\text{ mA}$; $I_B = 43\text{ }\mu\text{A}$; $V_B = 0.7\text{ V}$; $V_C = 1.4\text{ V}$; $V_E = 0\text{ V}$

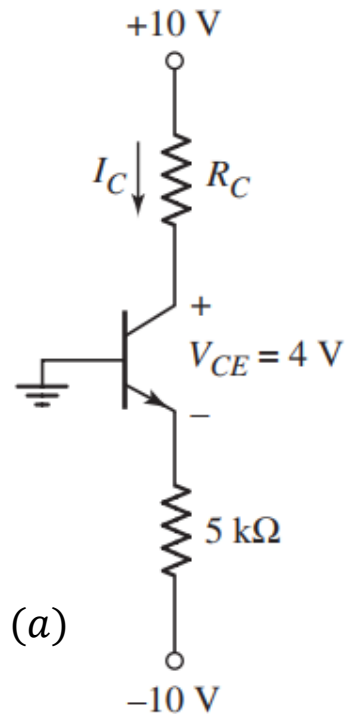Problem 4


- For the NPN transistors in the following circuit, $\beta = 75$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine the labeled quantities.



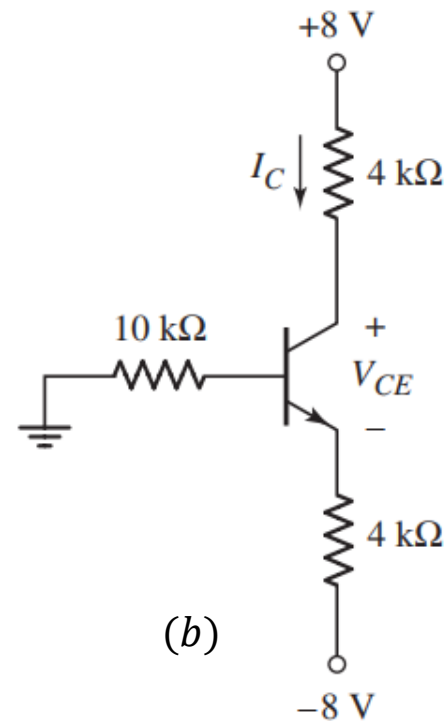Ans: Active; $I_C = 1.84\text{ mA}$; $I_E = 1.86\text{ mA}$; $I_B = 20\text{ }\mu\text{A}$; $V_B = 0\text{ V}$; $V_C = 3.3\text{ V}$; $V_E = -0.7\text{ V}$; $R_C = 3.64\text{ k}\Omega$



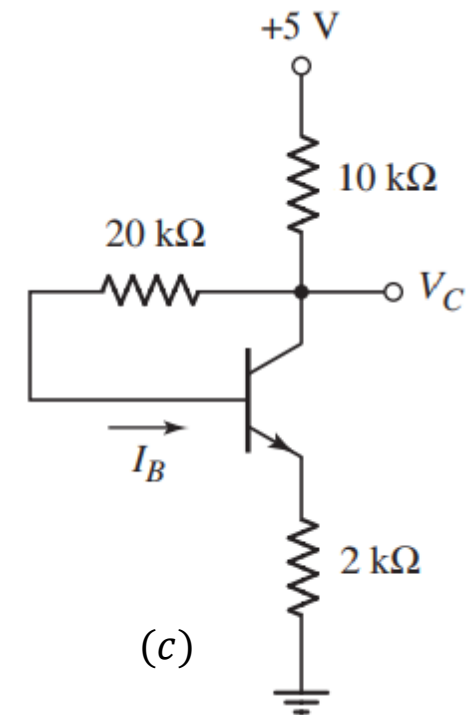
Ans: Active; $I_C = 1.725\text{ mA}$; $I_E = 1.76\text{ mA}$; $I_B = 35\text{ }\mu\text{A}$; $V_B = -0.26\text{ V}$; $V_C = 1.1\text{ V}$; $V_E = -0.96\text{ V}$




Ans: Active; $I_C = 0.341\text{ mA}$; $I_E = 0.346\text{ mA}$; $I_B = 5\text{ }\mu\text{A}$; $V_B = 1.4\text{ V}$; $V_C = 1.54\text{ V}$; $V_E = 0.7\text{ V}$

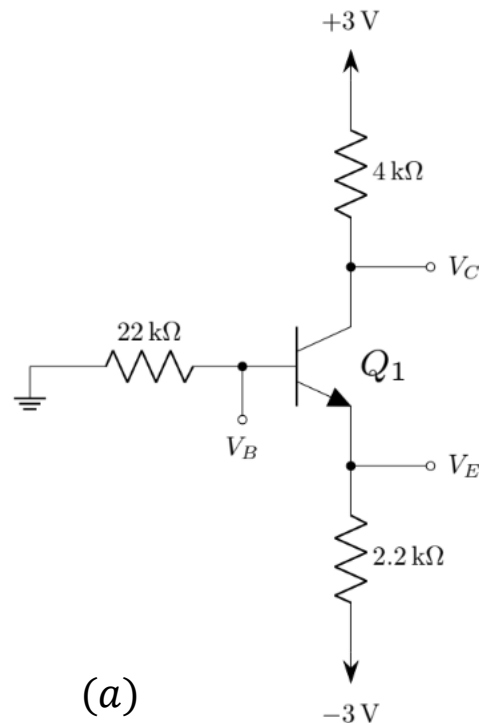Problem 5

- For the transistors in the following circuits, $\beta = 100$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine V_B , V_C , and V_E . [Hint for (b): $V_{BC} = V_{BE} - V_{CE}$]



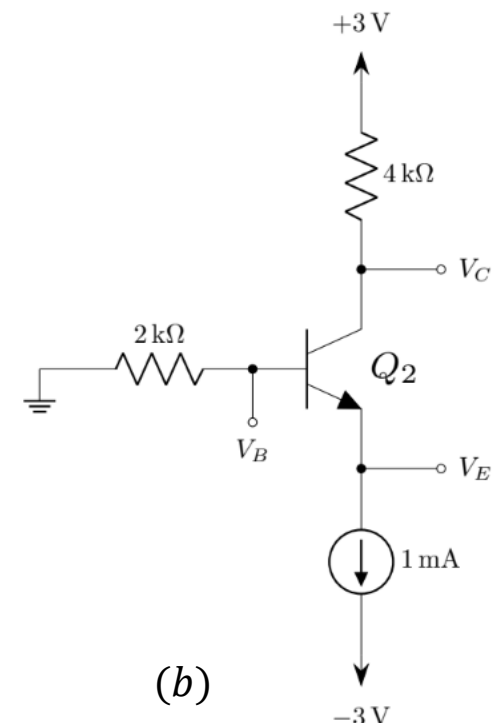
Ans: Sat; $I_C = 0.933\text{ mA}$; $I_E = 0.9394\text{ mA}$; $I_B = 6.1\text{ }\mu\text{A}$; $V_B = -0.13\text{ V}$; $V_C = -0.732\text{ V}$; $V_E = -0.93\text{ V}$



Ans: Sat; $I_C = 0.933\text{ mA}$; $I_E = 1\text{ mA}$; $I_B = 0.067\text{ mA}$; $V_B = -0.134\text{ V}$; $V_C = -0.732\text{ V}$; $V_E = -0.934\text{ V}$

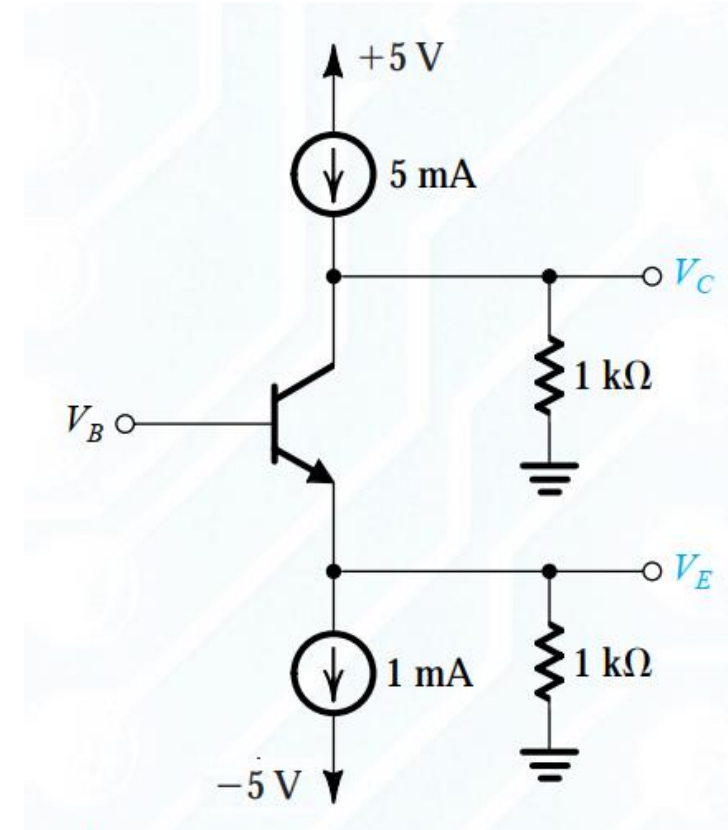Problem 6

- For the adjacent circuit, assume that $V_{BE} = 0.7\text{ V}$. For what value of V_B does the transistor operates in cut-off?



Ans: $I_C = I_B = I_E = 0$; $V_B = 0.3\text{ V}$; $V_C = 5\text{ V}$; $V_E = -1\text{ V}$


Problem 7

- For the adjacent circuit, assume that V_{BE} remains constant at 0.7 V when the transistor is ON. The transistor β is specified to be 50. Determine the value of V_{BB} that results in the transistor operating:

- in the active region with $V_{CE} = 5\text{ V}$,
- at the edge of saturation, and

[Hint: at the edge of saturation, β is still 50 and assume $V_{CE} = 0.3\text{ V}$.]

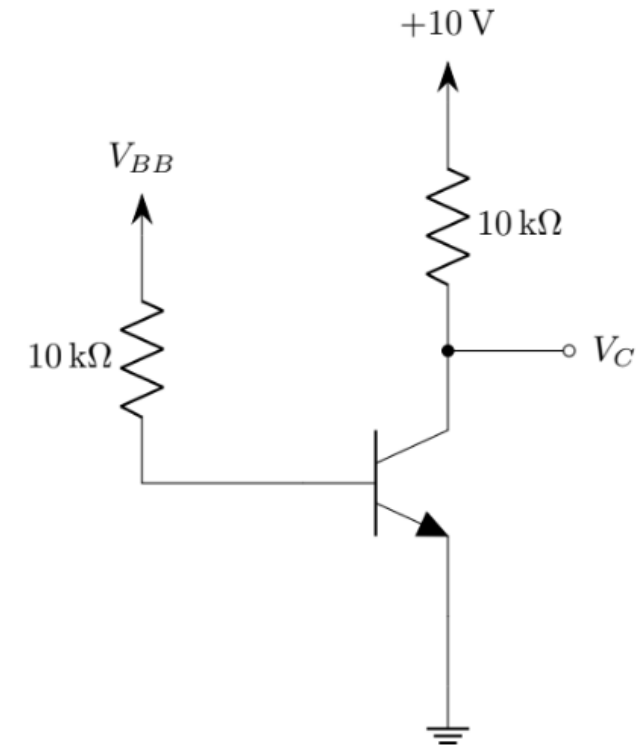- deep in saturation with $\beta_{forced} = 10$ and $V_{CE} = 0.2\text{ V}$.



Ans: I. $I_C = 0.5\text{ mA}$; $I_E = 0.51\text{ mA}$; $I_B = 10\text{ }\mu\text{A}$; $V_B = 0.7\text{ V}$; $V_C = 5\text{ V}$; $V_E = 0\text{ V}$; $V_{BB} = 0.8\text{ V}$

Ans: II. $I_C = 0.97\text{ mA}$; $I_E = 0.9894\text{ mA}$; $I_B = 19.4\text{ }\mu\text{A}$; $V_B = 0.7\text{ V}$; $V_C = 0.3\text{ V}$; $V_E = 0\text{ V}$; $V_{BB} = 0.894\text{ V}$

Ans: III. $I_C = 0.98\text{ mA}$; $I_E = 1.076\text{ mA}$; $I_B = 98\text{ }\mu\text{A}$; $V_B = 0.7\text{ V}$; $V_C = 0.2\text{ V}$; $V_E = 0\text{ V}$; $V_{BB} = 1.68\text{ V}$

Problem 8

- For the following circuit, $V_S = 5\text{ V}$, $R_L = 10\text{ k}\Omega$, and $R_I = 500\text{ k}\Omega$. Assume $\beta = 100$ for the transistor, $V_{BE, active} = V_{BE, sat} = 0.6\text{ V}$, and $V_{CE, at the edge of sat} = V_{CE, sat} = 0.2\text{ V}$.

I. Derive an expression relating v_O and v_I assuming the transistor is in active mode.

Ans: $v_O = 6.2 - 2v_I$

II. What is the highest value of v_I for which the transistor operates in cut-off.


Ans: 0.6 V

III. What is the highest (or lowest) value of v_I for which the transistor operates in its active region (or enters into its saturation region). What are the corresponding range for v_O ? [$\beta = 100$ at the edge of saturation]

Ans: 3 V

IV. Based on the relation found in I and values of v_I and v_O found in II and III, draw the VTC (v_O vs. v_I) graph for the circuit.

$$\text{Ans: } v_O = \begin{cases} 5\text{ V}, & v_I \leq 0.6\text{ V}, \text{ Cutoff} \\ 6.2 - 2v_I, & 0.6\text{ V} < v_I \leq 3\text{ V}, \text{ Active} \\ 0.2\text{ V}, & v_I > 3\text{ V}, \text{ Saturation} \end{cases}$$

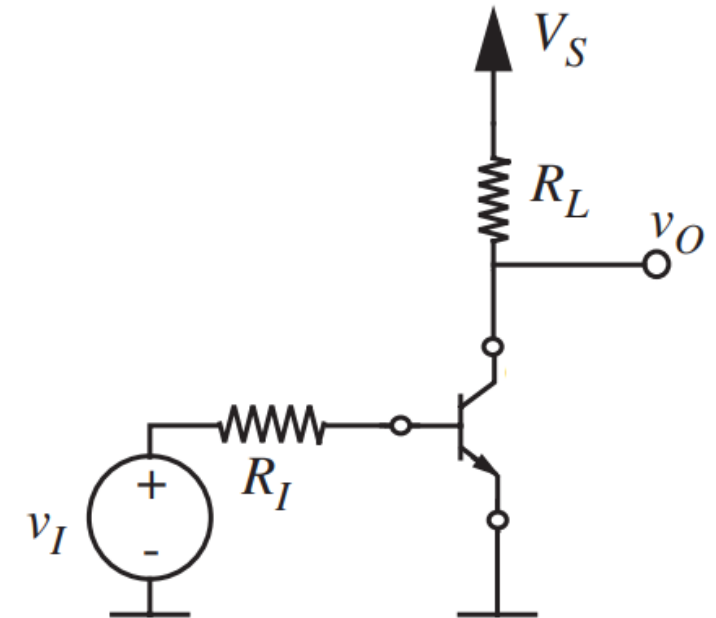

Problem 9

- For the following circuit, $V_S = 10\text{ V}$, $R_E = 100\text{ k}\Omega$, and $R_I = 10\text{ k}\Omega$. Assume $\beta = 100$ for the transistor, $V_{BE, active} = V_{BE, sat} = 0.6\text{ V}$, and $V_{CE, at edge of sat} = V_{CE, sat} = 0.2\text{ V}$.

I. Derive an expression relating v_O and v_I assuming the transistor is in active mode.

Ans: $v_O \approx v_I - 0.6$

II. What is the highest value of v_I for which the transistor operates in cut-off.


Ans: 0.6 V

III. What are the highest (or lowest) values of v_I for which the transistor remains in its active region (or operates at the edge of saturation). What are the corresponding range for v_O ? [$\beta = 100$ at the edge of saturation]

Ans: 10.4 V


IV. Based on the expression found in I and values of v_I and v_O found in II and III, draw the VTC (v_O vs. v_I) graph for the circuit.

$$\text{Ans: } v_O = \begin{cases} 0\text{ V}, & v_I \leq 0.6\text{ V}, \text{ Cutoff} \\ v_I - 0.6, & 0.6\text{ V} < v_I \leq 10.4\text{ V}, \text{ Active} \\ 9.8\text{ V}, & v_I > 10.4\text{ V}, \text{ Saturation} \end{cases}$$

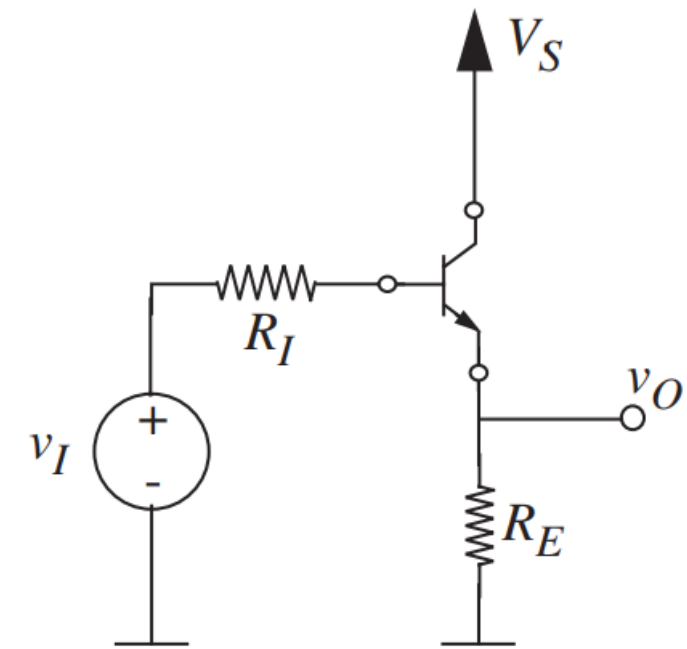

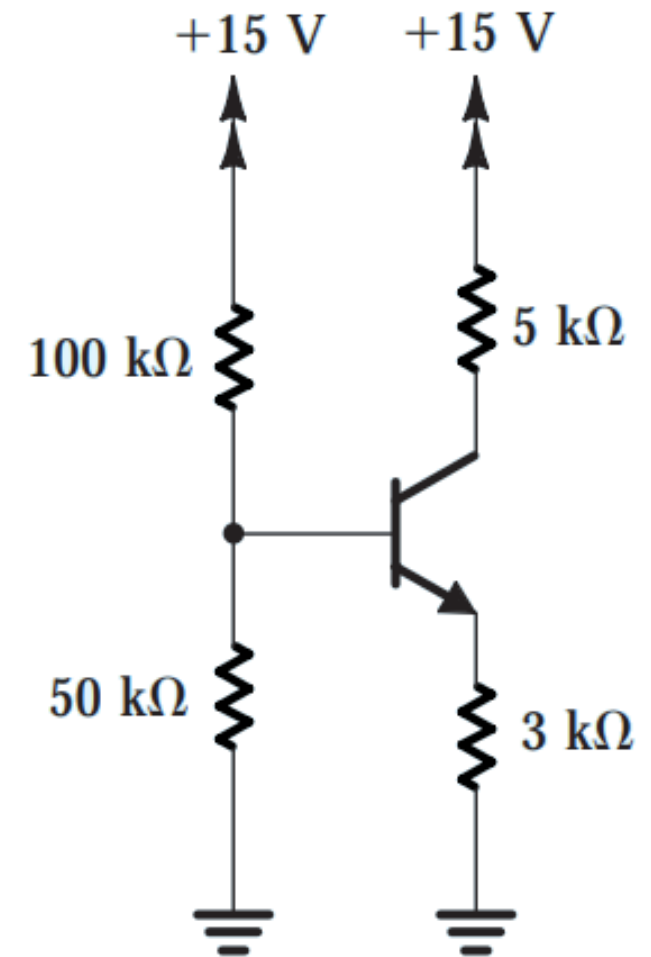Problem 10


- For the NPN transistor in the following circuit, $\beta = 100$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine the current through the $50\text{ k}\Omega$ resistor.



Ans: *Active*; $I_C = 1.28\text{ mA}$; $I_E = 1.2928\text{ mA}$; $I_B = 12.8\text{ }\mu\text{A}$; $V_B = 4.58\text{ V}$; $V_C = 8.6\text{ V}$; $V_E = 3.88\text{ V}$; *Current through $50\text{ k}\Omega = 91.6\text{ }\mu\text{A}$*

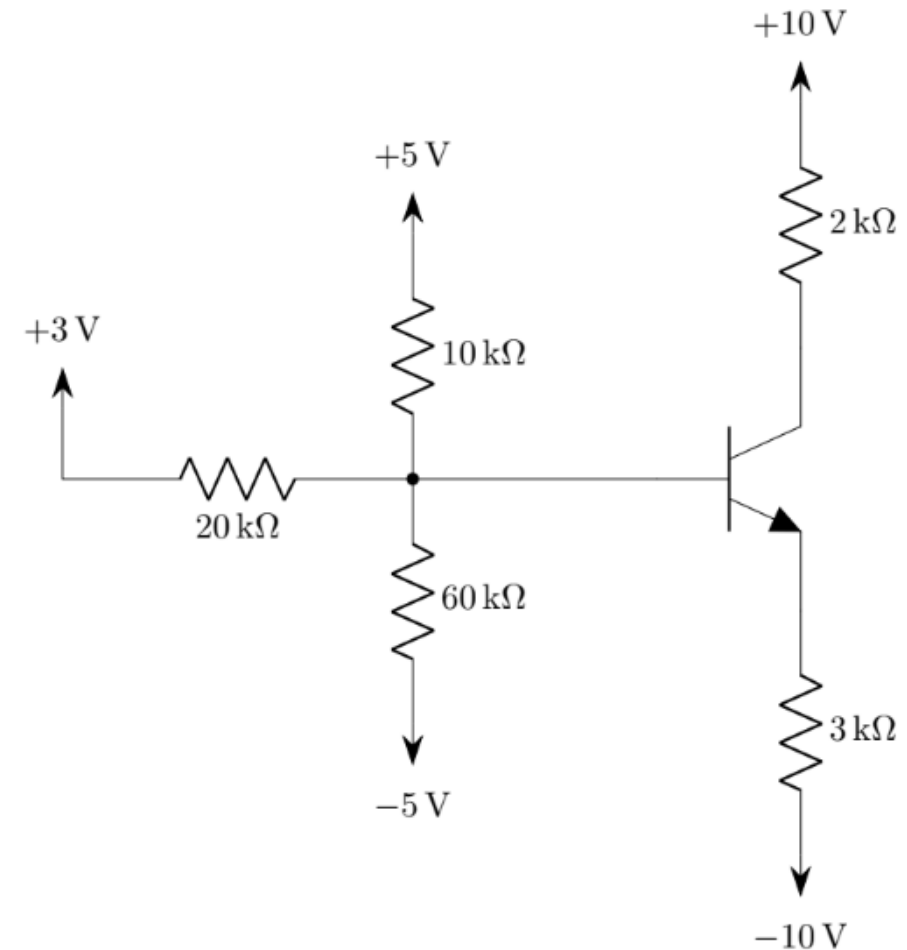Problem 11


- For the NPN BJT in the adjacent circuit, $\beta = 100$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine the operating region of the transistor.



Ans: *Sat*; $I_C = 3.9\text{ mA}$; $I_E = 4\text{ mA}$; $I_B = 0.1\text{ mA}$; $V_B = 2.8\text{ V}$; $V_C = 2.2\text{ V}$; $V_E = 2\text{ V}$

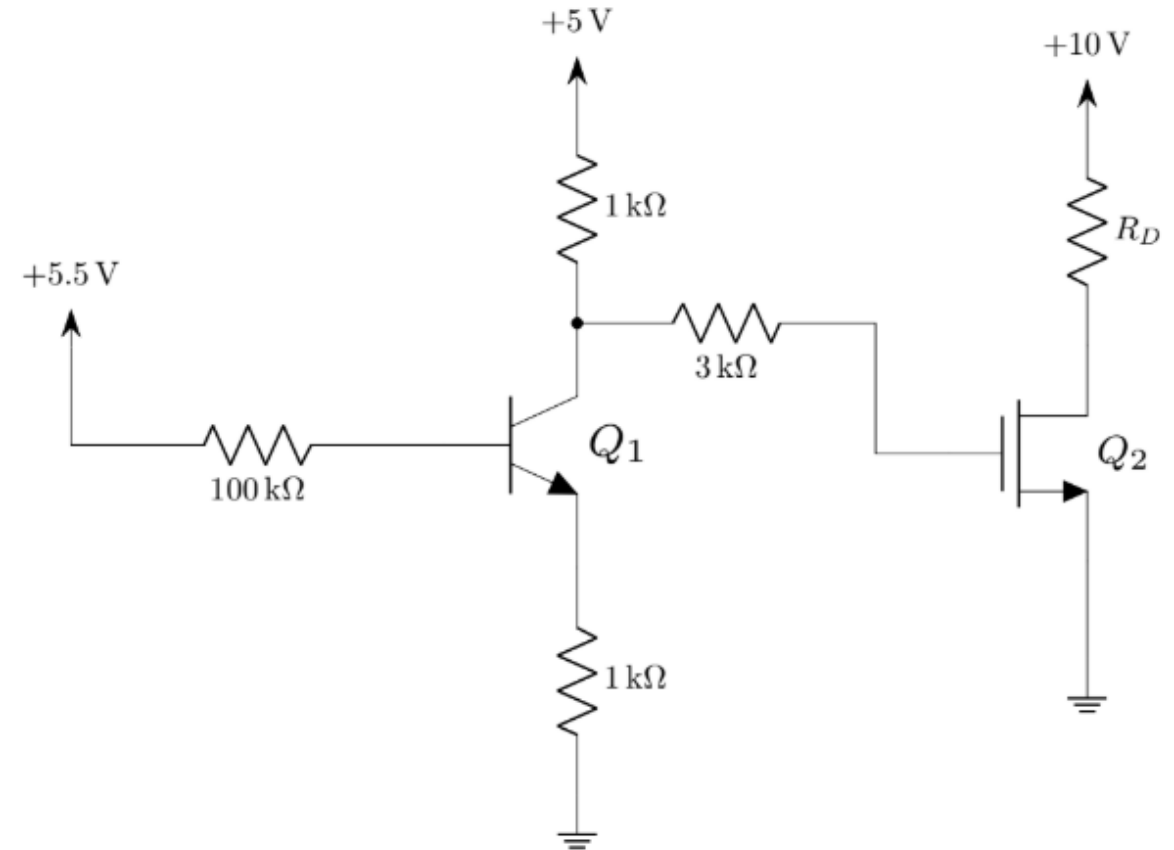Problem 12

- For the transistor Q_1 in the adjacent circuit, $\beta = 100$, V_{BE} is constant at 0.7 V when Q_1 remains ON, and $V_{CE,sat} = 0.2\text{ V}$. For Q_2 , $k'_n = 0.25\text{ mA/V}^2$, $\left(\frac{W}{L}\right) = \frac{0.72\text{ }\mu\text{m}}{0.18\text{ }\mu\text{m}}$, and $V_{Tn} = 1\text{ V}$. Determine the value of R_D so that Q_2 operates at the edge of saturation.




Ans: Q_1 : Active; $I_C = 2.39\text{ mA}$; $I_E = 2.4139\text{ mA}$; $I_B = 23.9\text{ }\mu\text{A}$; $V_B = 3.11\text{ V}$; $V_C = 2.61\text{ V}$; $V_E = 2.4139\text{ V}$

Ans: Q_2 : $V_G = 2.61\text{ V}$; $V_D = 1.61\text{ V}$; $I_{DS} = 1.2961\text{ mA}$; $R_D \approx 7\text{ k}\Omega$

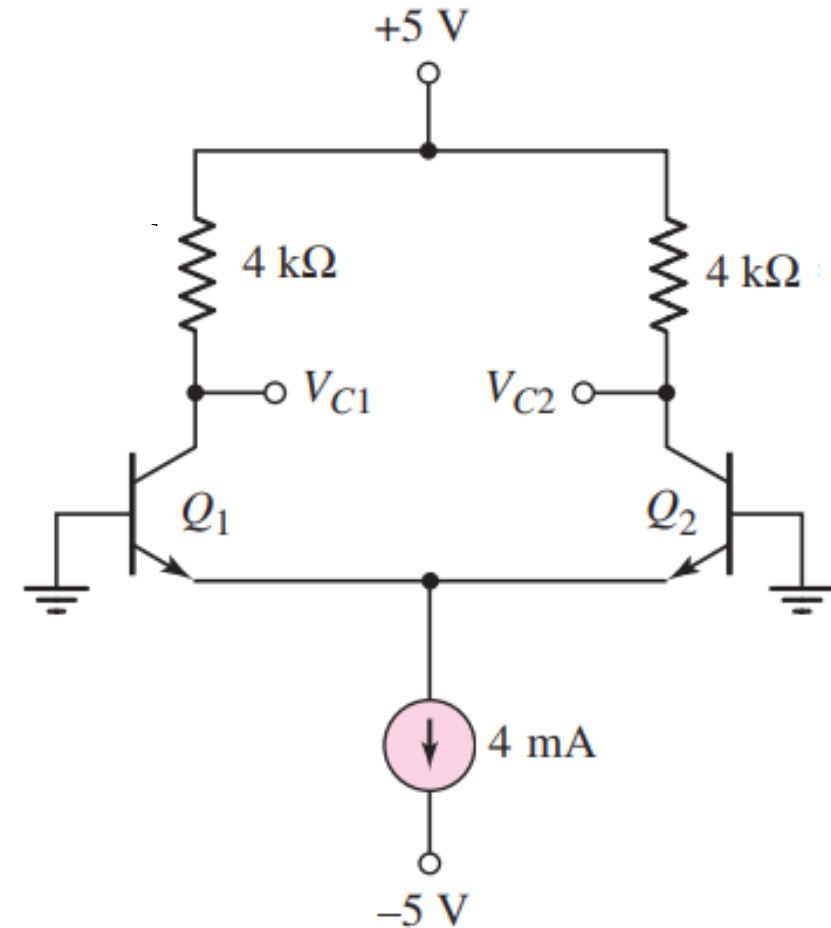Problem 13


- The transistors in the adjacent circuit are identical. Here, $\beta = 100$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine V_{C1} and V_{C2} .



Ans: Both Q_1 & Q_2 are in Sat Mode; $I_{E1} = I_{E2} = 2\text{ mA}$; $V_{B1} = V_{B2} = 0\text{ V}$; $V_{E1} = V_{E2} = -0.8\text{ V}$; $V_{C1} = V_{C2} = -0.6\text{ V}$; $I_{C1} = I_{C2} = 1.4\text{ mA}$; $I_{B1} = I_{B2} = 0.6\text{ mA}$

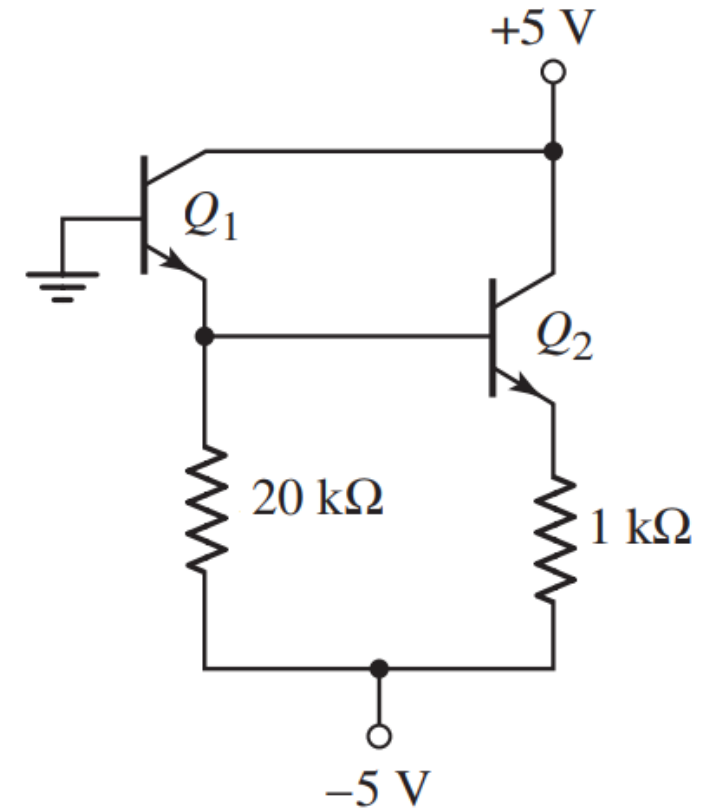Problem 14


- The transistors in the following circuit are identical. Here, $\beta = 80$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.7\text{ V}$, and $V_{CE, sat} = 0.2$. Determine the base currents.



Ans: Both Q_1 & Q_2 are in Active Mode; $V_{B_1} = V_{B_2} = 0\text{ V}$; $V_{E_1} = V_{E_2} = -0.7\text{ V}$; $I_{E_1} = I_{E_2} = 0.215\text{ mA}$; $I_{B_1} = I_{B_2} = 2.7\text{ }\mu\text{A}$; $V_{C_1} = V_{C_2} = 5\text{ V}$; $I_{C_1} = I_{C_2} = 0.212\text{ mA}$

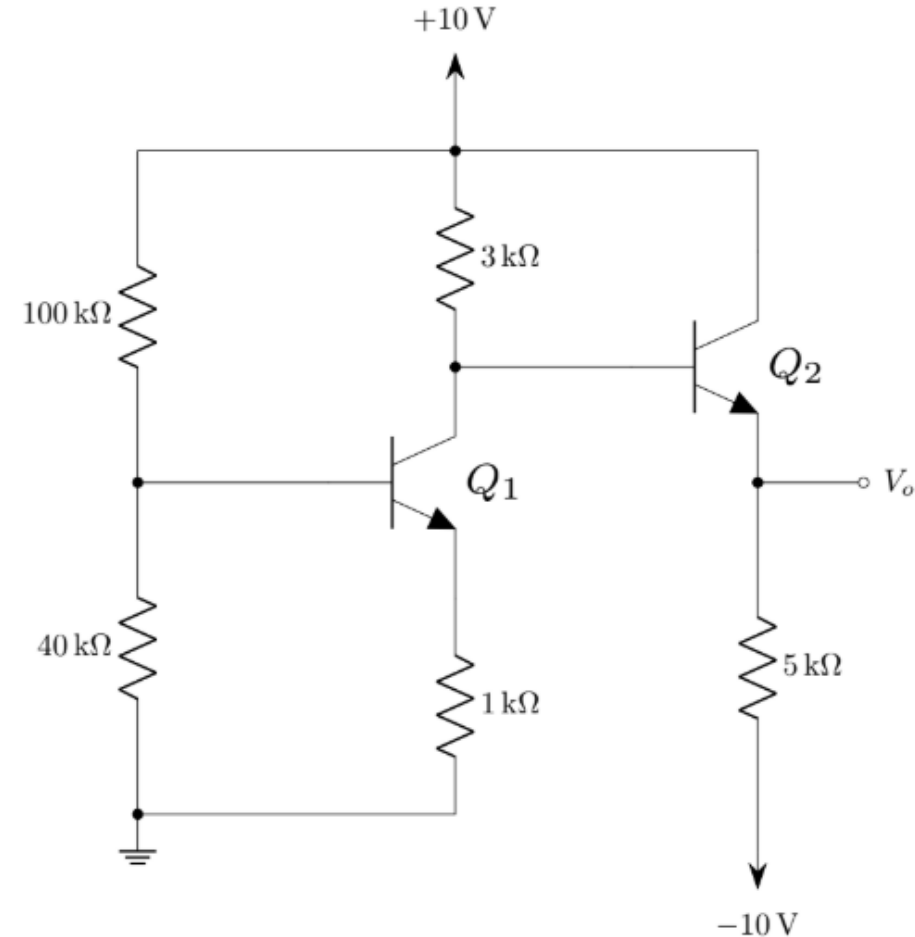Problem 15

- The transistors in the adjacent circuit are identical. Here, $\beta = 120$, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.7\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine V_o .



Ans: Q_1 is in Active Mode; $I_{B1} = 0.0238\text{ mA}$; $I_{C1} = 2.856\text{ mA}$; $I_{E1} = 2.88\text{ mA}$; $V_{E1} = 2.88\text{ V}$; $V_{B1} = 3.58\text{ V}$; $V_{C1} = V_{B2} = 1.41\text{ V}$; Q_2 is in Active Mode; $V_{C2} = 10\text{ V}$; $I_{B2} = 0.0177\text{ mA}$; $I_{C2} = 2.124\text{ mA}$; $I_{E2} = 2.1417\text{ mA}$; $V_{E2} = V_o = 0.71\text{ V}$; $V_{B2} = V_{C1} = 1.41\text{ V}$

Up Next

Relevant *Questions* from Past Semesters

Final — Fall 2025 - 1/2

- The transistors Q_2 and Q_3 in the following circuit are identical and have the parameters given in the box.
 - Determine V_1 and V_2 .
 - Determine V_3 and I_{DS} .

NPN BJT Parameters:

For the transistor Q_2 ,

Common emitter current gain: $\beta = 100$

Base-emitter voltage in the active region:

$$V_{BE(active)} = 0.7 \text{ V}$$

Base-emitter voltage in the saturation region:

$$V_{BE(sat)} = 0.8 \text{ V}$$

Collector-emitter voltage in the saturation region:


$$V_{CE(sat)} = 0.2 \text{ V}$$

N-Channel MOSFET Parameters:

For the transistor Q_3 ,

Threshold voltage: $V_{T_n} = 1 \text{ V}$

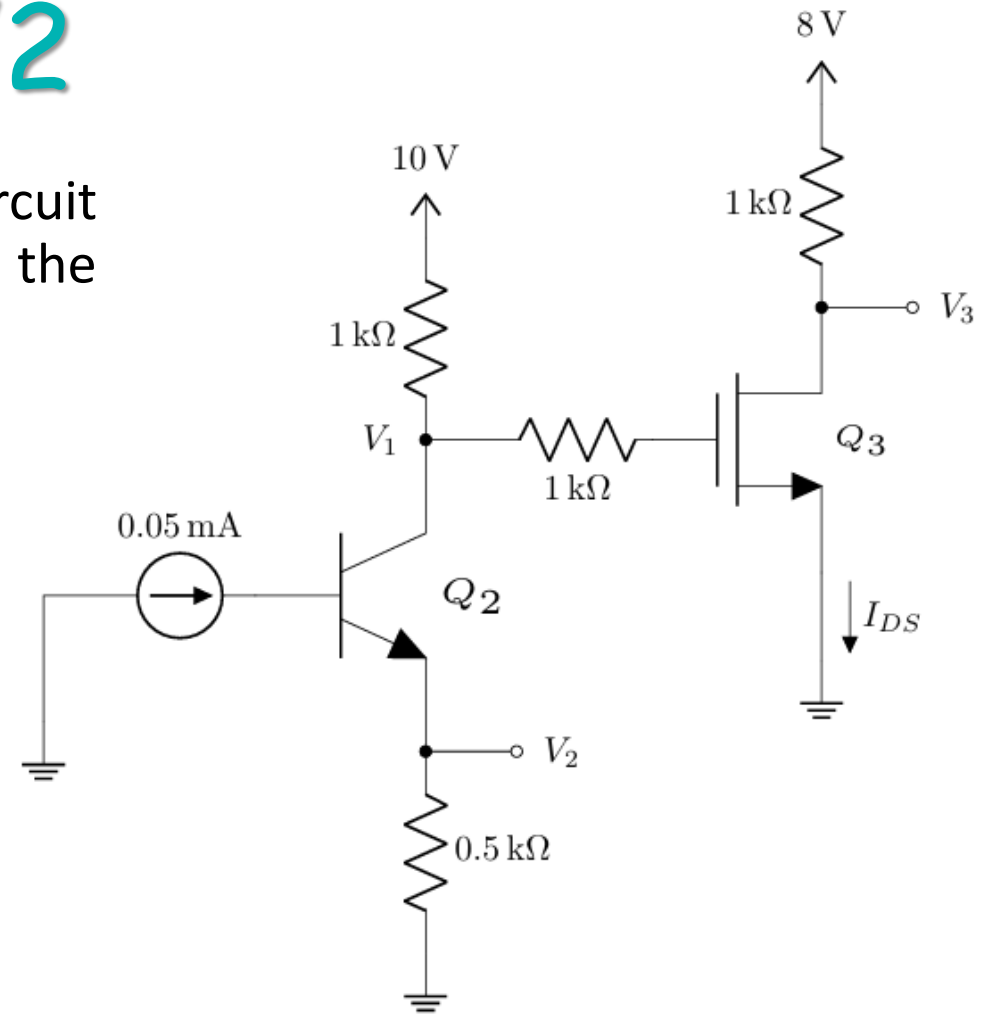Transconductance parameter: $k_n = 2 \text{ mA/V}^2$



Ans: (a) $Q_2 \rightarrow \text{Active}$; $V_1 = 5 \text{ V}$; $V_2 = 2.525 \text{ V}$
(b) $Q_3 \rightarrow \text{Triode}$; $V_3 = 1 \text{ V}$; $I_{DS} = 7 \text{ mA}$

Final — Fall 2025 - 2/2

The output voltage v_O for the circuit shown below is plotted as a piecewise function of the input voltage v_I . The different regions of transistor operation are indicated by vertical dashed lines, and the specific transistor parameters are provided in the accompanying box.

- When the transistor operates at the edge of saturation, the emitter current is $I_E = 3.94 \text{ mA}$. Determine the values of R_L and R_I . [Use $\beta = 100$]
- Using the values found in part (a), what is the value of I_E when $v_I = 5 \text{ V}$.



NPN BJT Parameters:

For the transistor Q_4 ,

Common emitter current gain: $\beta = 100$

Base-emitter voltage: $V_{BE(sat)} = V_{BE(active)} \approx 0.6 \text{ V}$

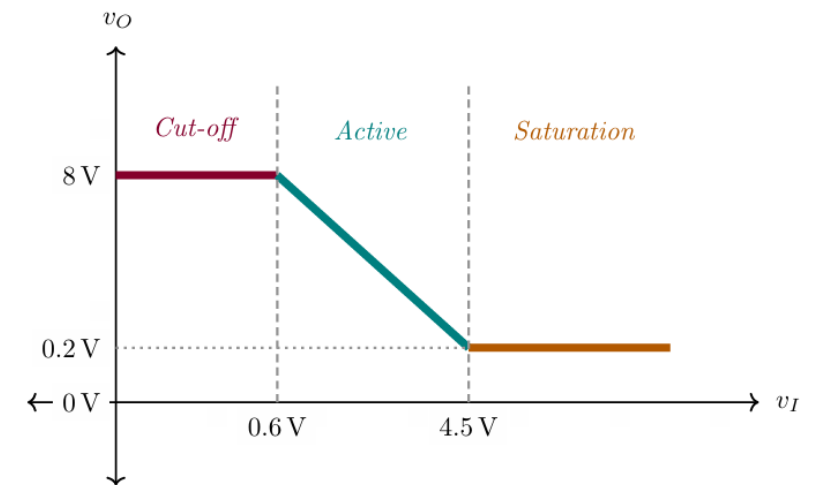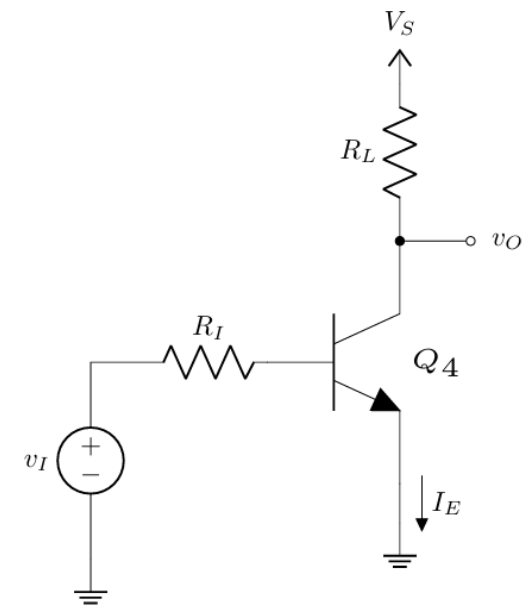
Collector-emitter voltage: $V_{CE(sat)} = V_{CE(edge \text{ of } sat)} \approx 0.2 \text{ V}$



Ans: (a) $R_I = 100 \text{ k}\Omega$; $R_L = 2 \text{ k}\Omega$
(b) $I_E = 3.944 \text{ mA}$; $I_B = 0.044 \text{ mA}$; $I_C = 3.9 \text{ mA}$

Final — Summer 2025

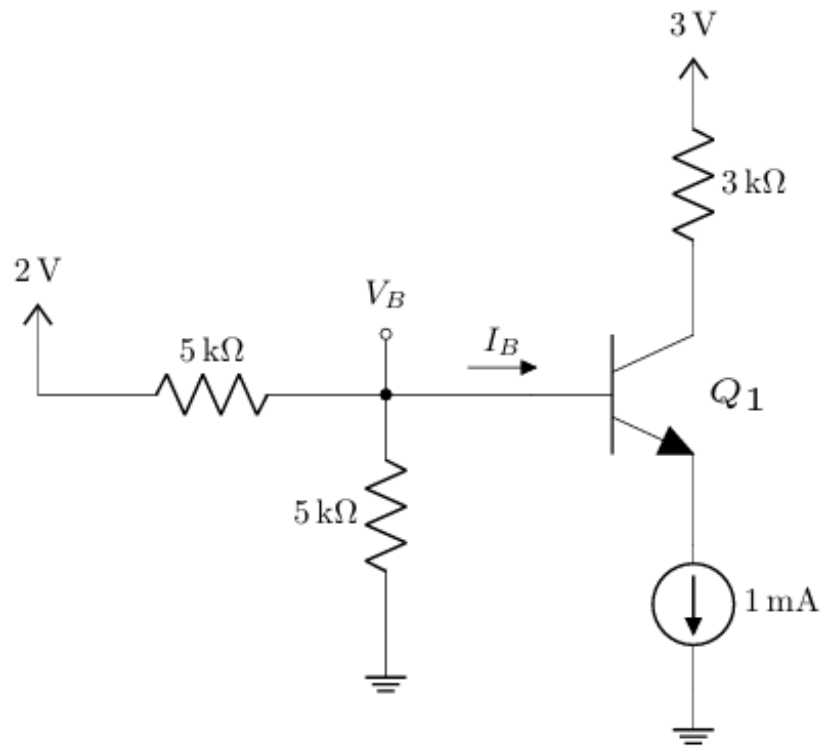- Verify that Q_1 operates in the saturation region, and determine all terminal currents and voltages of the transistor.



NPN BJT Parameters:

For the transistor Q_1 :

Current gain: $\beta = 100$


Base-emitter voltage in saturation: $V_{BE(sat)} = 0.8\text{ V}$

Collector-emitter voltage in saturation: $V_{CE(sat)} = 0.2\text{ V}$

Ans: Sat; $I_C = 0.927\text{ mA}$; $I_E = 1\text{ mA}$; $I_B = 0.073\text{ mA}$; $V_B = 0.818\text{ V}$; $V_C = 0.218\text{ V}$; $V_E = 0.018\text{ V}$

Final — Spring 2025

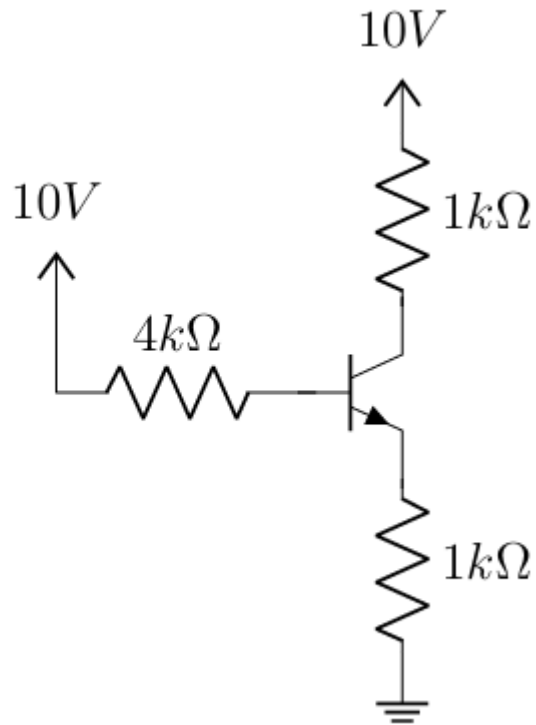- Analyze the circuit below, and calculate I_B , I_C , I_E , V_C , and V_E using the method of assumed states. You must validate your assumption.



NPN BJT Parameters:

For the transistor Q_1 :

Current gain: $\beta = 100$

Base-emitter voltage in saturation: $V_{BE(sat)} = 0.8\text{ V}$

Collector-emitter voltage in saturation: $V_{CE(sat)} = 0.2\text{ V}$

Ans: *Sat*; $I_C = 4.42\text{ mA}$; $I_E = 5.38\text{ mA}$; $I_B = 0.96\text{ mA}$; $V_B = 6.18\text{ V}$; $V_C = 5.58\text{ V}$; $V_E = 5.38\text{ V}$

Final — Fall 2024

- Analyze the circuit below, and calculate I_B , I_C , I_E , and V_O using the method of assumed states. You must validate your assumption.


NPN BJT Parameters:

For the transistor Q_1 :

Current gain: $\beta = 100$

Base-emitter voltage in saturation: $V_{BE(sat)} = 0.8\text{ V}$


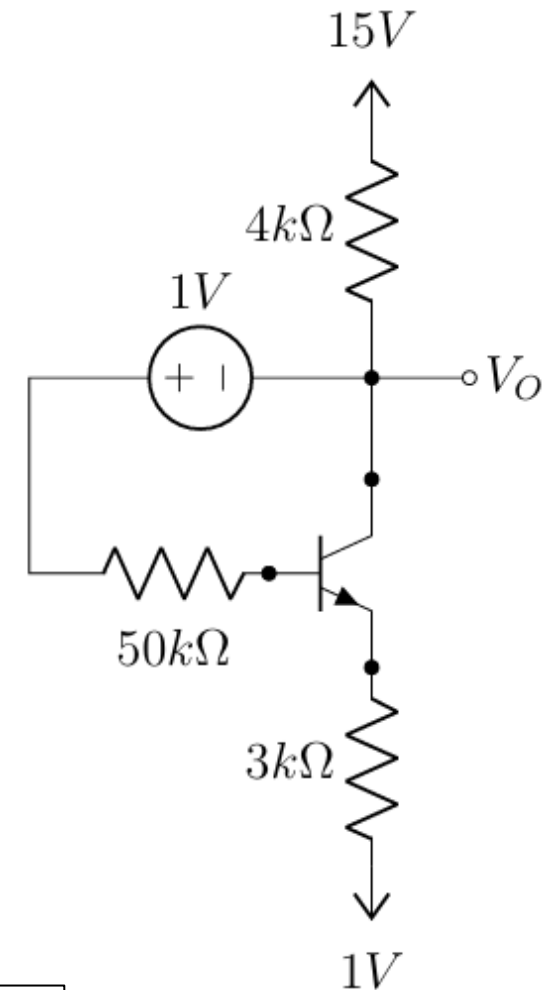
Collector-emitter voltage in saturation: $V_{CE(sat)} = 0.2\text{ V}$



Ans: Active; $I_C = 1.89\text{ mA}$; $I_E = 1.908\text{ mA}$; $I_B = 0.0189\text{ mA}$; $V_B = 5.515\text{ V}$; $V_C = 5.46\text{ V}$; $V_E = 4.715\text{ V}$

Final — Summer 2024 - 1/2

- Karim designed a BJT circuit. When his friend Rahim saw it, he claimed that the BJT would operate in the Active mode. Then Rahim built a circuit and asked Karim to figure out the operating mode the BJT.
 - Calculate I_B , I_C , I_E , and V_{CE} in Karim's circuit and determine whether Rahim was correct or not.
 - Analyze Rahim's circuit and calculate I_B , I_C , I_E , and V_{CE} to help Karim determine the operating state of the BJT.

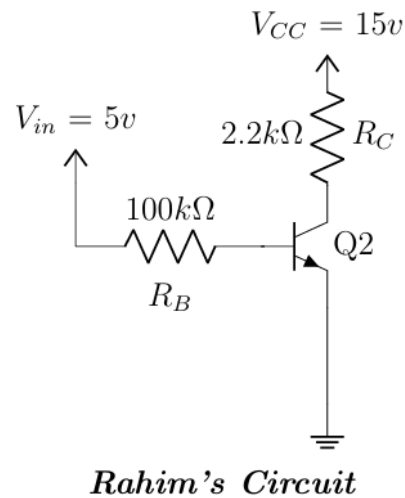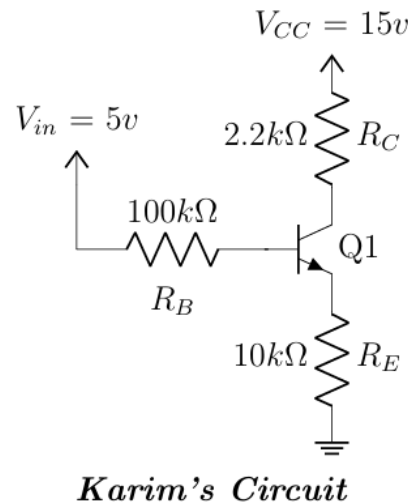

For Both BJTs
 $\beta = 100$
 $V_{BE(Active)} = 0.7v$
 $V_{BE(Saturation)} = 0.8v$
 $V_{CE(Saturation)} = 0.2v$

Ans: (a) Active; $I_C = 0.3874 \text{ mA}$; $I_E = 0.391 \text{ mA}$; $I_B = 3.874 \mu\text{A}$; $V_B = 4.61 \text{ V}$; $V_C = 14.15 \text{ V}$; $V_E = 3.91 \text{ V}$
(b) Active; $I_C = 4.3 \text{ mA}$; $I_E = 4.343 \text{ mA}$; $I_B = 0.043 \text{ mA}$; $V_B = 4.61 \text{ V}$; $V_C = 5.54 \text{ V}$; $V_E = 0 \text{ V}$

Final — Summer 2024 - 2/2

- Analyze the circuit below, and calculate I_B , I_C , I_E , and V_{CE} using the method of assumed states. You must validate your assumption.


BJT Parameters

$$\beta = 90$$

$$V_{BE(Active)} = 0.7v$$

$$V_{BE(Saturation)} = 0.8v$$


$$V_{CE(Saturation)} = 0.2v$$

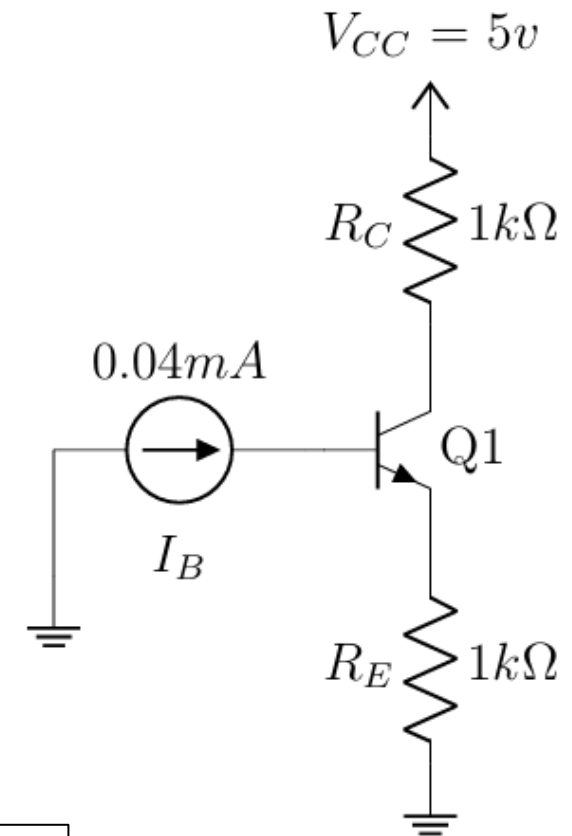

Ans: Sat; $I_C = 4.93 mA$; $I_E = 4.9825 mA$; $I_B = 0.0525 mA$; $V_B = 5.7825 V$; $V_C = 5.46 V$; $V_E = 4.715 V$

Final — Spring 2024 - 1/2

- Andrew and Nicole found the adjacent circuit built in a trainer board. From the transistor model, they knew it had a gain of $\beta = 80$. Additionally, $V_{BE, active} = 0.7\text{ V}$, $V_{BE, sat} = 0.7\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. They also saw $V_{CC} = 5\text{ V}$, $R_B = 2\text{ k}\Omega$, and $R_C = 3\text{ k}\Omega$. However, the R_E resistor was an unknown one. So, they provided an input of $V_{in} = 2\text{ V}$ and measured the output to be $V_O = 2.2\text{ V}$. Nicole said, “In this condition, the transistor is in active mode”. But, Andrew disagreed.
 - Design the circuit, i.e., determine the value of R_E , using what Nicole said about the mode of the transistor.
 - Using the value of R_E obtained from (a), determine who will be right if $V_{in} = 4\text{ V}$.

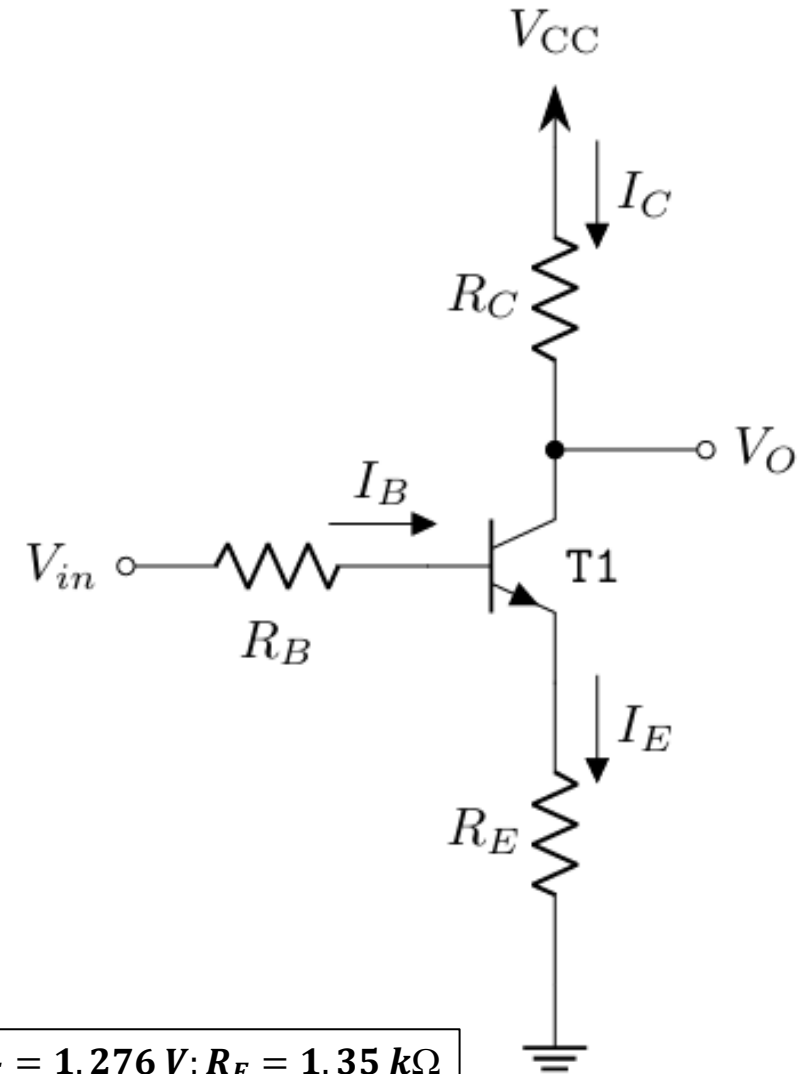


Ans: (a) $I_C = 0.933\text{ mA}$; $I_E = 0.945\text{ mA}$; $I_B = 0.012\text{ mA}$; $V_B = 1.976\text{ V}$; $V_C = V_O = 2.2\text{ V}$; $V_E = 1.276\text{ V}$; $R_E = 1.35\text{ k}\Omega$
(b) Sat; $I_C = 0.912\text{ mA}$; $I_E = 1.53\text{ mA}$; $I_B = 0.618\text{ mA}$; $V_B = 2.766\text{ V}$; $V_C = V_O = 2.264\text{ V}$; $V_E = 2.066\text{ V}$;

Final — Spring 2024 - 2/2

- For the adjacent circuit,
 - Find out the currents going through the three terminals of the transistor Q1.
 - Determine the value of V_1 and V_2 .
 - Design the circuit, i.e. find an appropriate value of R_D , such that Q2 remains at the edge of saturation, i.e., when $V_{DS} = V_{GS} - V_T$.

the value of V_1 and V_2 .

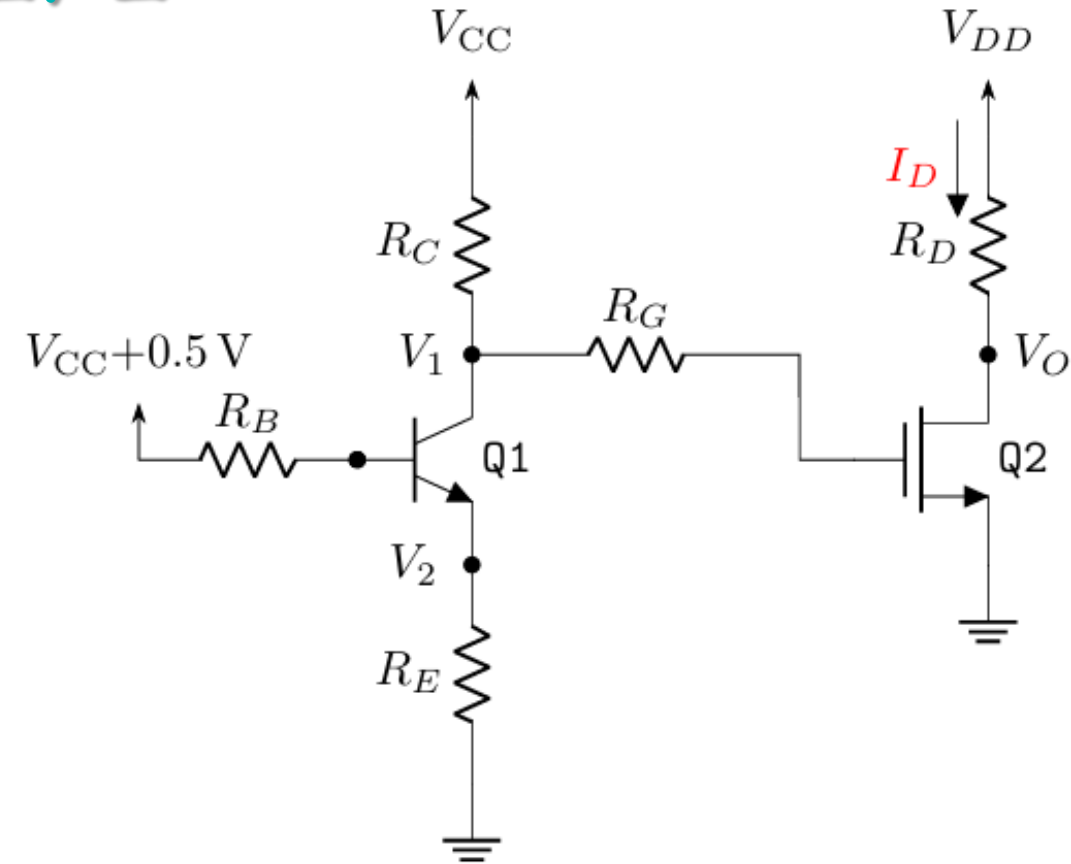circuit, i.e. find an appropriate value of R_D , such that Q2 remains at the edge of saturation, i.e., when $V_{DS} = V_{GS} - V_T$.




Ans: (a) Sat; $I_C = 2.27 \text{ mA}$; $I_E = 2.295 \text{ mA}$; $I_B = 0.025 \text{ mA}$; $V_B = 3 \text{ V}$
 (b) $V_1 = V_C = 2.503 \text{ V}$; $V_2 = V_E = 2.295 \text{ V}$
 (c) $V_D = 1.5 \text{ V}$; $R_D = 7.556 \text{ k}\Omega$

Resistor values in ($\text{k}\Omega$)					Supply Voltages	
R_B	R_C	R_E	R_G	R_D	$V_{CC} = 5 \text{ V}$	$V_{DD} = 10 \text{ V}$
100	1.1	1	3	-		

Final — Fall 2023

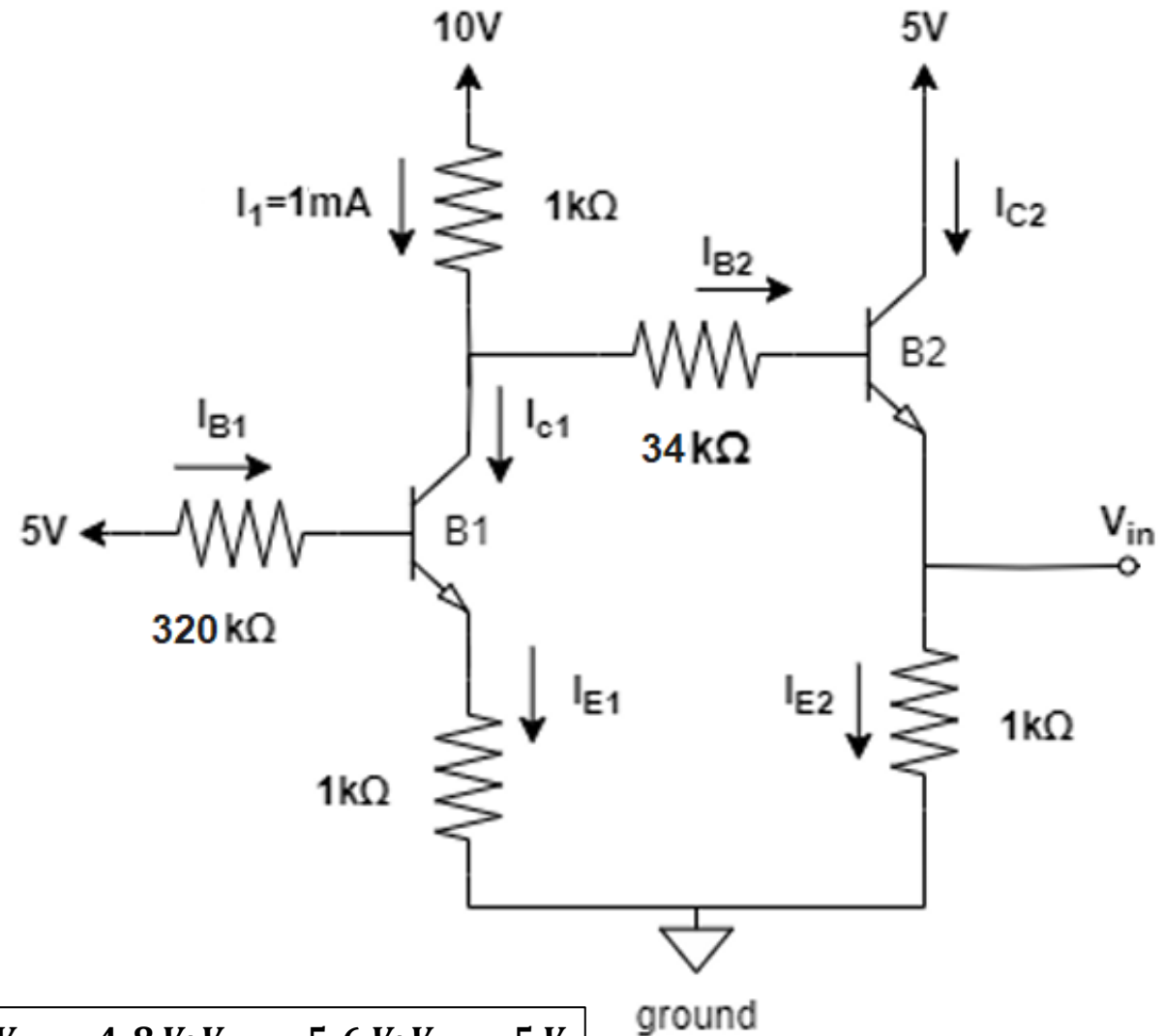
- The BJTs in the following circuit have parameters: $\beta = 75$, $V_{BE, active} = V_{BE, sat} = 0.8\text{ V}$, and $V_{CE, sat} = 0.2\text{ V}$. Determine the operating regions of B_1 and B_2 .



Ans: $B2 \rightarrow Sat$; $I_{E2} = 4.8\text{ mA}$; $I_{C2} = 4.7\text{ mA}$; $I_{B2} = 0.1\text{ mA}$; $V_{E2} = 4.8\text{ V}$; $V_{B2} = 5.6\text{ V}$; $V_{C2} = 5\text{ V}$
 $B1 \rightarrow Active$; $I_{E1} = 0.912\text{ mA}$; $I_{C1} = 0.9\text{ mA}$; $I_{B1} = 0.012\text{ mA}$; $V_{E1} = 0.912\text{ V}$; $V_{B1} = 1.16\text{ V}$; $V_{C1} = 9\text{ V}$

Final — Summer 2023

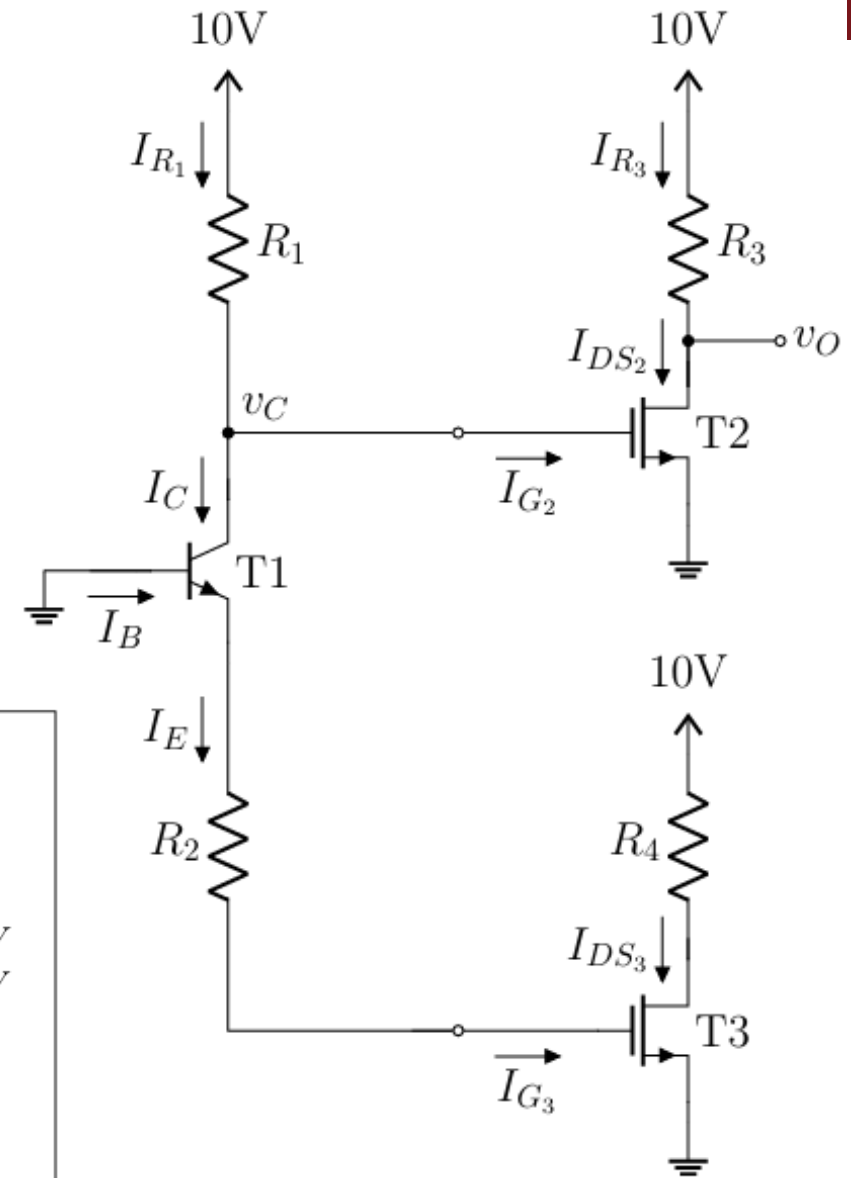- For the adjacent circuit, $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$, and $R_4 = 4\text{ k}\Omega$.
 - Determine the values of I_C , I_B , I_E , and v_C of T1.
 - Determine the value of I_{DS_2} and v_O of T2.



for BJT

$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(\text{Active})} = 0.7\text{V}$$

$$v_{BE(\text{Saturation})} = 0.8\text{V}$$

$$v_{CE(\text{Saturation})} = 0.2\text{V}$$

for MOSFET

$$V_T = 1\text{V}$$

$$k = 5\text{mA/V}^2$$

Ans: T1 → Cutoff; $I_E = I_B = I_C = 0\text{ mA}$; $v_C = 10\text{ V}$; $V_E > 0.8\text{ V}$; $V_B = 0\text{ V}$;

T3 → Curoff; $I_{DS_2} = 0\text{ mA}$; $I_{G_3} = 0\text{ mA}$

T2 → Triode; $I_{G_2} = 0\text{ mA}$; $I_{DS_2} = 3.31\text{ mA}$; $v_O = V_D = 0.074\text{ V}$

Final — Spring 2023 - 1/3

- Analyze the following circuit to find the values of i_B , i_C , i_E , and v_{CE} . Assume saturation mode and validate the assumptions.


$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(Active)} = 0.7V$$

$$v_{BE(Saturation)} = 0.8V$$


$$v_{CE(Saturation)} = 0.2V$$

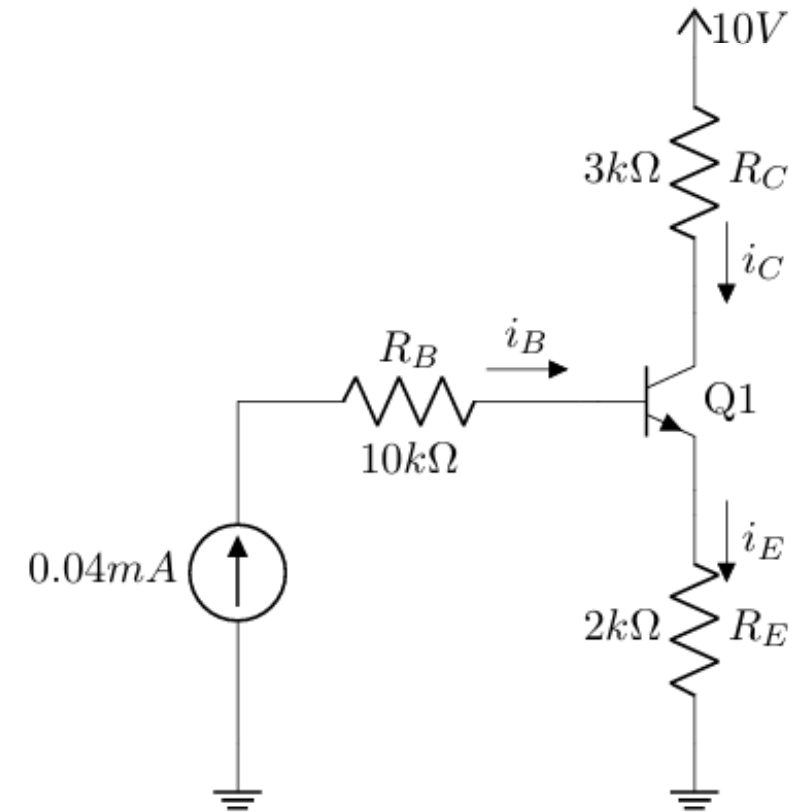

Ans: Sat; $i_C = 1.944 \text{ mA}$; $i_E = 1.984 \text{ mA}$; $i_B = 0.04 \text{ mA}$; $V_B = 4.768 \text{ V}$; $V_C = 4.168 \text{ V}$; $V_E = 3.968 \text{ V}$

Final — Spring 2023 - 2/3

- The transistors in the following circuit have parameters: $k_n = 5 \text{ mA/V}^2$, $V_{Tn} = 0.7 \text{ V}$, $\beta = 85$, $V_{BE, active} = 0.7 \text{ V}$, $V_{BE, sat} = 0.8 \text{ V}$, and $V_{CE, sat} = 0.2 \text{ V}$.
 - Find out the operating mode of the MOSFET. *[Hint: You don't need to solve the circuit to proof that.]*
 - Calculate I_{DS} and V_{DS} using the given parameters.
 - Determine V_1 , I_B , I_C , and I_E .

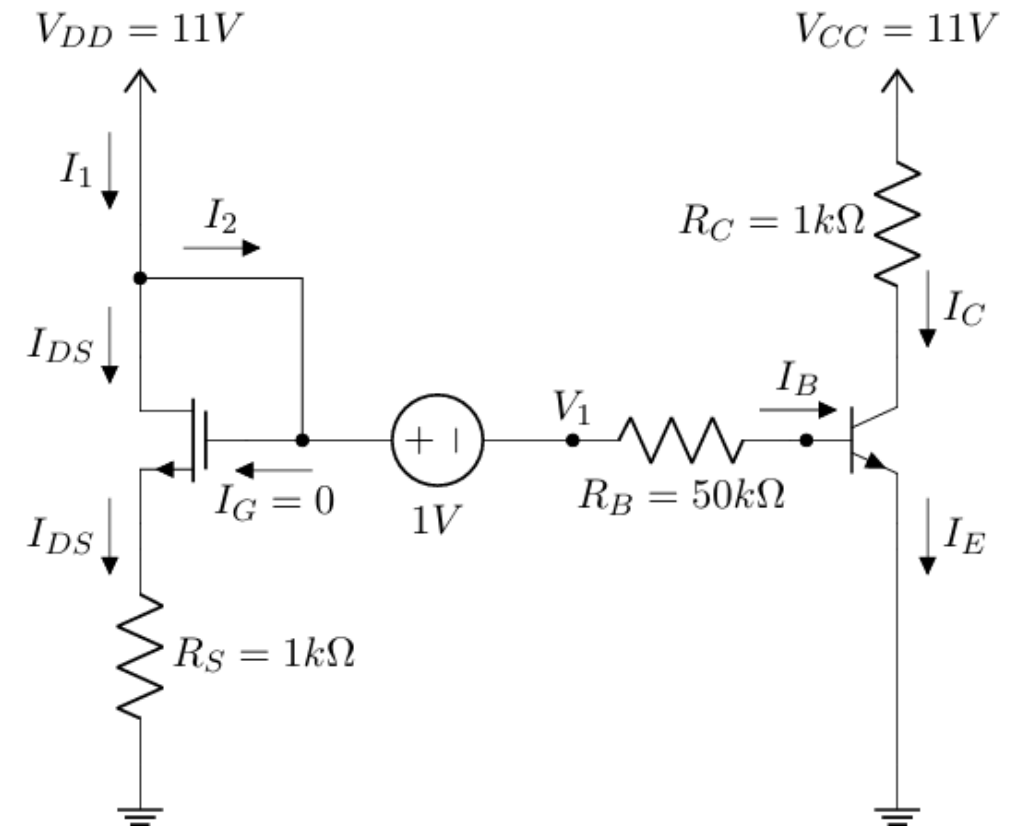


Ans: (b) Sat; $I_{DS} = 8.46 \text{ mA}$; $V_{DS} = 8.46 \text{ V}$

(c) Sat; $V_1 = 10 \text{ V}$; $I_B = 0.184 \text{ mA}$; $I_C = 10.8 \text{ mA}$; $I_E = 10.984 \text{ mA}$; $V_C = 0.2 \text{ V}$; $V_B = 0.8 \text{ V}$; $V_E = 0 \text{ V}$



Final — Spring 2023 - 3/3

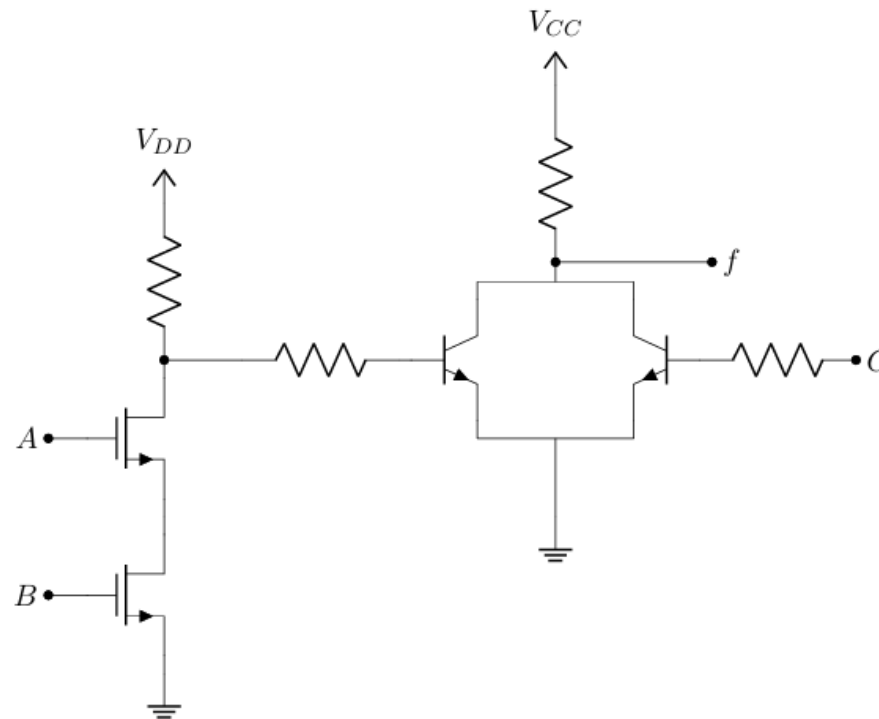- a. For the logic circuit (b), write an expression for the Boolean output f in terms of the Boolean inputs A , B , and C .



Final — Fall 2022

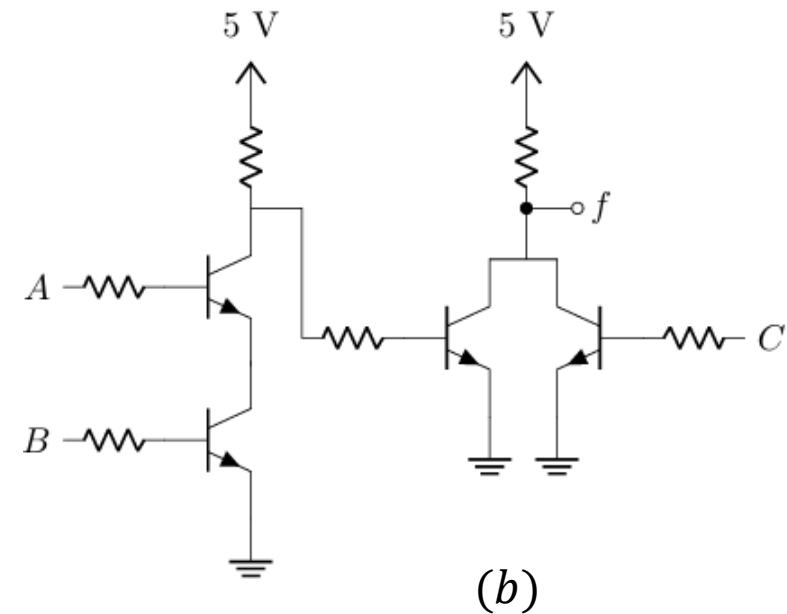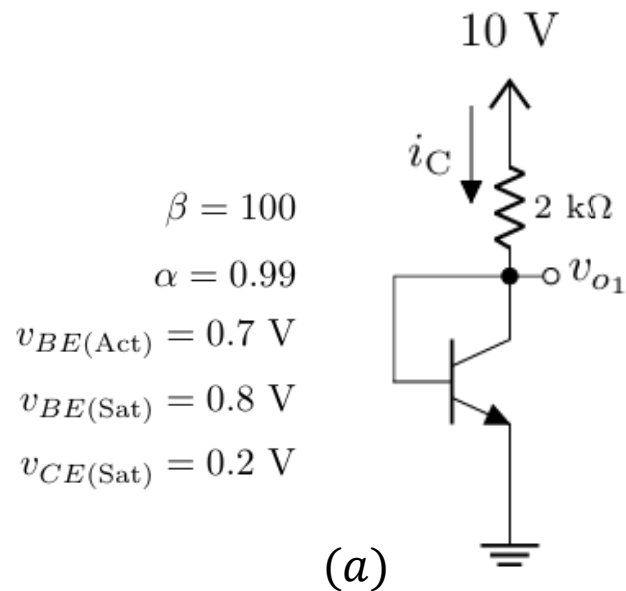
- Analyze the circuit (a) to find i_C and v_{o1} using the Method of Assumed State. Validate your assumptions.
- For the logic circuit (b), write an expression for the Boolean output f in terms of the Boolean inputs A , B , and C .



Ans: (a) Active; $i_C = 4.65 \text{ mA}$; $i_E = 4.6965 \text{ mA}$; $I_B = 0.0465 \text{ mA}$; $V_B = V_C = v_{o1} = 0.7 \text{ V}$; $V_E = 0 \text{ V}$

Final — Summer 2022

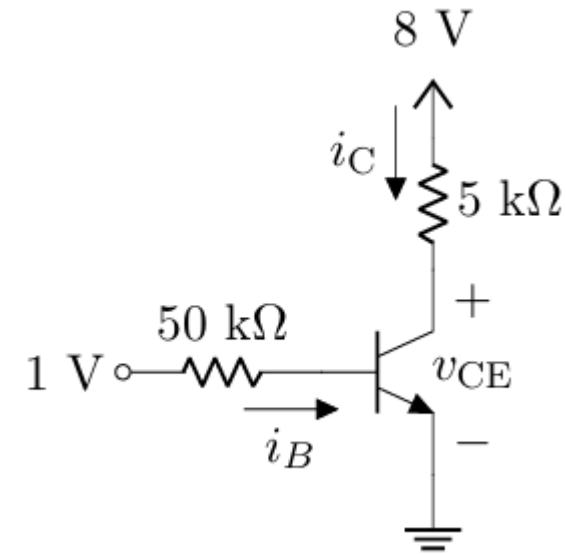- Analyze the adjacent circuit to find i_C and v_{CE} using the Method of Assumed State. Validate your assumptions.



$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(\text{Active})} = 0.7 \text{ V}$$

$$v_{BE(\text{Saturation})} = 0.8 \text{ V}$$

$$v_{CE(\text{Saturation})} = 0.2 \text{ V}$$

Ans: Active; $i_C = 0.6 \text{ mA}$; $i_E = 0.6006 \text{ mA}$; $I_B = 0.006 \text{ mA}$; $V_B = 0.7 \text{ V}$; $V_E = 0 \text{ V}$; $V_C = V_{CE} = 5 \text{ V}$

Acknowledgement and References

Some of the problems in this set are taken or adapted from the following sources:

1. Agarwal, A. and Lang, J., Foundations of Analog and Digital Electronic Circuits, Morgan Kaufmann
2. Sedra, A. S., & Smith, K. C., Microelectronic Circuits, Oxford University Press
3. Neamen, D. A., Microelectronics: Circuit Analysis and Design, McGraw-Hill